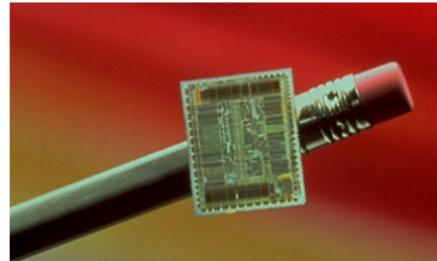




INSTITUT  
Mines-Télécom



# ICS904/EN2 : Design of Digital Integrated Circuits

L2 : Structural design of digital circuits  
(1/2))

Yves MATHIEU

[yves.mathieu@telecom-paristech.fr](mailto:yves.mathieu@telecom-paristech.fr)






# Integrated logic

- How to build logic functions with electronic components ?
- Many possible implementations ...
  - derived from the manipulation of logical expressions.
  - derived from component properties (MOS transistors, bipolar ...)
- Arbitrary choice of a physical variable to represent the logic states
- Many paths explored in the years 70-90
- Major classes of solutions stabilized since.
- But research still continues ...



 
# CMOS inverter

- The selected supply voltage is the reference for defining the Boolean signal
- Harnessing the symmetrical behavior of NMOS and PMOS transistors.



# The 2 input NAND gate

 

## NMOS network


- ON if the two NMOS transistors are "ON"
- OFF if one of the two NMOS transistors is "OFF"

a	b	Output
0	0	1
0	1	1
1	0	1
1	1	0

## PMOS network

- ON if one of the two PMOS transistors is "ON"
- OFF if the two PMOS transistors are "OFF"

# The two input NOR gate

 

## NMOS network

- ON if one of the two NMOS transistor is "ON"
- OFF if the two NMOS transistors are "OFF"

a	b	Output
0	0	1
0	1	0
1	0	0
1	1	0

## PMOS network

- ON if the two PMOS transistors are "ON"
- OFF if One of the two PMOS transistor is "OFF"

# CMOS logic

## Generalization to other boolean functions

- Given the truth-table of boolean function.
- PMOS networks are used for the logic ones of the boolean function.
- NMOS networks are used for the logic zeros of the boolean function.
- A one to one NMOS/PMOS structure
- Implementable gates have a function of the form
$$F(x_0, x_1, \dots, x_n) = \overline{\sum \prod x_i}$$
- Other boolean functions are assemblies of these primitive gates.

# CMOS logic

Construction methods for functions of the form  $F = \sum \prod x_i$

- First, build the NMOS network :

- Express the  $F(x_0, x_1, \dots, x_n)$  function in the form  $\sum \prod x_i$
- Perform any factorisation/simplification.
- Remaining  $\prod$  match with series of NMOS transistors (or network of NMOS transistors).
- Remaining  $\sum$  match with NMOS transistors (or network of NMOS transistors) connected in parallel.

# CMOS logic

Construction methods for functions of the form  $F = \sum \prod x_i$

## ■ Second, build the PMOS network :

- Express the  $F(x_0, x_1, \dots, x_n)$  function in the form  $\sum \prod \bar{x}_i$
- Perform any factorisation/simplification.
- Remaining  $\prod$  match with series of PMOS transistors (or network of PMOS transistors).
- Remaining  $\sum$  match with PMOS transistors (or network of PMOS transistors connected in parallel).


## ■ Two remarks :

- Simplest CMOS gates are inverting gates (NAND is smaller than AND)
- Dual PMOS and NMOS networks may be used :
  - Use parallel PMOS network when series of NMOS networks are used
  - Use series of PMOS network when parallel NMOS networks are used
- This latter method often leads to a non optimal gate (from electrical point of view)


 
## CMOS logic


$$Z = \overline{A \cdot B + C \cdot (D + E)}$$



# CMOS logic

Optimum network :  $F = \overline{A} \cdot B + B \cdot C + A \cdot \overline{C}$

 - **Q1** : Build the gate using optimum optimisation methods
- **Q2** : Exchange "C" NMOS transistor with "A/B" NMOS network : Does it make any difference ?
- **Q3** : Build the gate using dual PMOS and NMOS networks
- **Q4** : What are the potential flaws of this later gate ?





# CMOS logic


## Low/High input counts

- Series of transistors : the body effect (see lecture L1) leads to slow high  $V_t$  transistors.
- Assembly of low input count gates may be faster than high input counts gates.
- AND6 gate example, 28nm process, 1v supply voltage, all NMOS transistors of equal size,  $w_p/w_n = 1.6$ , no output load.
- Test cases : (1) All inputs change, (2) One input changes.
- Q1 : Setup a simple model of propagation type, using resistive approximation

■ NAND6+INV	■ NAND3+NOR2	■ NAND2+NOR3
■ $T_{p1R} = 53\text{ps}$	■ $T_{p1R} = 29\text{ps}$	■ $T_{p1R} = 27\text{ps}$
■ $T_{p1F} = 18\text{ps}$	■ $T_{p1F} = 5\text{ps}$	■ $T_{p1F} = 4\text{ps}$
■ $T_{p2R} = 33\text{ps}$	■ $T_{p2R} = 19\text{ps}$	■ $T_{p2R} = 18\text{ps}$

# CMOS logic

## non complementary PMOS/NMOS networks

 


- NMOS and PMOS networks may be simultaneously OFF.
- Usage : Input/Output tranceivers for external busses.
- Tristate invertor.

EN	A	Z
0	0	highZ
0	1	highZ
1	0	1
1	1	0

# CMOS logic

## non complementary PMOS/NMOS networks

 

- NMOS and PMOS networks may be simultaneously ON.
- Taking into account input cases, short-circuits are avoided.
- Only for full custom design (not included in automated methods)

A	B	Z
0	0	1
0	1	forbidden case
1	0	High Z
1	1	0



- Logic style mainly used in standard cell libraries (see lecture L3)
  - Robustness, Noise immunity
  - The sizing of transistors affects only performance, not functionality.
  - In practical cases series of transistors are limited to 3 to 4 transistors :

# Why a so complicated structure ?

- Only one boolean function but two transistor networks ...
- Truth table of the boolean function :
  - The PMOS network generates the "1" values of the truth table
  - The NMOS network generates the "0" values of the truth table
- Only one network should be enough :
  - The "1" values of the truth table could be implicit values.
  - CMOS logic is not optimal from the standpoint of the complexity.

# Pass Transistor Logic


An ideal switch

  

- NMOS transistor efficient for falling transitions.
- PMOS transistor efficient for rising transitions.
- Warning : Passive circuit, no signal regeneration along the path "IN" to "OUT"
 
# Pass transistor logic


Input signals may be constants or variables



- Input is a constant : CMOS logic
- Input is a variable : Pass logic
- Combination of conditions and inputs should not lead to short-circuits.
- Combination of conditions and inputs should not lead to open-circuits.
- Any form of the Boolean expression.

# Pass Transistor Logic


## Full decoding

 

- $F = P_1 \cdot A \cdot B + P_2 \cdot A \cdot \bar{B} + P_3 \cdot \bar{A} \cdot B + P_4 \cdot \bar{A} \cdot \bar{B}$
- Division of the truth table into four sub-tables  
(P1, P2, P3, P4) based on the full decoding of the 2 inputs A and B.

# Pass Transistor Logic


Area minimization for constant inputs

 


- Constant zero is a connection to  $V_{ss}$
- Constant one is a connection to  $V_{dd}$
- Beware the inverted condition for the PMOS transistor

# Pass Transistor Logic
 
## Application to two input boolean functions





$$F = A \cdot X + \bar{A} \cdot Y$$

 

- F function is a simple mux between X and Y.
- Q1 : Generate the  $F = A + B$  function.
- Q2 : Compare the five functions with CMOS Logic.

# Pass Transistor Logic



## Trees of muxes

  

- $F1 = \bar{B} \cdot (\bar{A} \cdot X + A \cdot Y) + B \cdot (\bar{A} \cdot Z + A \cdot T)$
- $F2 = B \cdot A \cdot C + B \cdot \bar{A}$
- Less transistors than Pass Transistor Logic using decoders.
- But less simplifications (branch sharing)
- Heavily used for look-up tables (LUTs) in FPGAs.

# Pass Transistor Logic



## Non exclusive conditions

  

- Several branches may be simultaneously ON.
- Short circuits and High Impedance state should be avoided.
- $F : (C_1 = C_2) \Rightarrow A = B$

# Pass Transistor Logic

Two inputs XOR gate

  

- XOR :  $A \cdot \bar{B} + \bar{A} \cdot B$
- F1 : Classical pass transistor logic XOR gate (8 transistors including invertors)
- F2 : Pass transistor logic XOR gate using non exclusive branches (6 transistors including invertors)

# Pass Transistor Logic

## Chains of pass transistor logic / versus chain of invertors

- Passive propagation.
- RC time accumulation
- Test condition : CMOS 28nm,  $V_{DD} = 1V$ .
- Test case 1 : 2 invertors separated by N pass gates.
- Test case 2 : 2 invertors separated by N invertors.

N	1	2	3	4	5	6	7
T <sub>p</sub> pass chain (ps)	7	11	17	24	32	42	53
T <sub>p</sub> inv chain (ps)	7	12	18	23	29	35	41

- Increasing delta propagation time (cumulative RC)
- Use invertors every 2 or 3 pass gate.

# Pass Transistor Logic

## Examples

- **Q1** : Design of a 2 inputs XOR gate
  - **Q1.1** : How many transistors in CMOS logic.
  - **Q1.2** : Compare with pass transistor logic.
- **Q2** : Ripple carry adder.
  - **Q2.1** : Design the boolean function computing the output carry of a "Full adder" using CMOS logic.
  - **Q2.2** : Optimize the carry propagation of a  $2N$ -bits ripple carry adder.
  - In a full-adder, the output carry may be calculated as follows :
    - $C_{OUT} = G + P \cdot C_{IN}$
    - With G (carry generation) :  $G = A \cdot B$
    - With P (carry propagation) :  $P = A \oplus B$
  - **Q2.3** : Design a boolean function computing the output carry using previous equations and pass transistor logic

# Pass Transistor Logic

## Summary

- Requires less transistors than CMOS logic ...
- Partially passive logic...
  - Requires buffers every 2 to 4 paths...
  - Performances of a gate alone are difficult to assess : Performance evaluation at the assembly level....
- Gate inputs are not only transistor Gates but also transistor Drains or Sources.
  - Input capacitor depends from the state of the pass gate....
- Preferred Use :
  - Big "full-custom" digital blocs optimized for speed...
  - Embedded inside CMOS standard-cells ("automated design")....