

ICS904/EN2 : Design of Digital Integrated Circuits

From the bases of CMOS digital circuits
to the economical choices...

Yves MATHIEU


yves.mathieu@telecom-paristech.fr



Building a logic gate


What do we need ?

 - A ground reference : V_{ss}
- A power supply : V_{dd}
- An electrical definition for logic values : $0 \equiv V_{ss}$, $1 \equiv V_{dd}$
- A resistive load : R_{load}
- A switch **controlled** by a voltage (referenced to V_{ss})
 - $V_{control} = 0$ Open switch
 - $V_{control} = V_{dd}$ Closed switch




Let's try to build a more complex gate ...

The two input NAND gate

 

Let's try other gates...

The two input NOR gate

 


Very simple structures

but...

- A permanent current flows through the gate when the logic output is **0** :
 - The only usefull power consumption should be linked to the **activity** of gates not to their state. . .
- Physicists do not know how to realize ideals switches (at reasonable operating temperatures) :
 - The **0** logic level doesn't reach V_{ss} .
 - Safe operation of the gate is not guaranteed.

The MOS transistor


Metal Oxide Semiconductor

 


CMOS transistors

Complementary Metal Oxide Semiconductor

 - Gate : G , Drain : D , Source : S , Threshold Voltage : V_T
- With $V_{TN} > 0$ and $V_{TP} < 0$



nMOS transistor

 


pMOS transistor

- | | |
|-----------------------------------|-----------------------------------|
| ■ N channel | ■ P channel |
| ■ Electrons current | ■ Holes current |
| ■ Conduction if $V_{gs} > V_{TN}$ | ■ Conduction if $V_{gs} < V_{TP}$ |

Simplistic model of the NMOS transistor

Schematic Symbols

 

Cut-off region

$$\text{If } V_{GS} \leq V_{TN} \text{ then } I_{DS} = 0$$

Conduction region (Saturation region)




$$\text{If } V_{GS} > V_{TN} \text{ then } I_{DS_{max}} = K_n \cdot (V_{GS} - V_{TN})^2$$

Technological and geometrical factors

$$K_n = \frac{1}{2} \mu_{0N} \cdot C'_{ox} \frac{W_N}{L_N}$$

Simplistic model of the PMOS transistor

Schematic symbols

   

Cut-off region

$$\text{If } V_{GS} \geq V_{TP} \text{ then } I_{DS} = 0$$


Conduction region (Saturation region)

$$\text{If } V_{GS} < V_{TP} \text{ then } I_{DS_{max}} = -K_p \cdot (V_{GS} - V_{TP})^2$$


Technological and geometrical factors

$$K_P = \frac{1}{2} \mu_{0P} \cdot C'_{ox} \frac{W_P}{L_P}$$

$$I_{DS} = f(V_{GS}, V_{DS})$$

 

28nm node. NMOS transistor

 



T_{ox} : gate oxide thickness




L : Gate Length



W : Gate Width


MOS transistors and logic levels

Two non ideal electronic switches

 

nMOS Transistor with Source connected to Ground.

 - $V_G = V_{ss}$
⇒ open switch
- $V_G = V_{dd}$
⇒ closed switch



pMOS Transistor with Source connected to power supply

- $V_G = V_{ss}$
⇒ closed switch
- $V_G = V_{dd}$
⇒ open switch

CMOS logic

CMOS inverter

■ Boolean input value $a = 0$

→ $V_a = 0$

→ nMOS cutoff

→ pMOS conducting

→ $V_z = V_{dd}$

→ boolean output value $z = 1$

■ boolean input value $a = 1$

→ $V_a = V_{dd}$


→ nMOS conducting

→ pMOS cutoff

→ $V_z = 0$


→ Boolean output value $z = 0$

 No static power consumption (first order approximation)



CMOS logic

The two input NAND gate

 


MOS switches efficiency

CMOS gates : parasitic capacitive loads

- Internal nodes of a logic gate have parasitic capacitances :
 - gate-source or gate-drain capacitance (gate oxide).
 - source-bulk ou drain-bulk capacitance (reverse biased diodes)
- The output of a logic gate is connected to :
 - Wires (parasitic capacitance to the ground, supply, or between nodes)
 - Inputs of other logic gates (transistors gate node)
- All these item may be summed to an equivalent unique parasitic capacitance C_{par} :
 - that should be charged during rising edges of the gate output
 - that should be discharged during falling edges of the gate output
- The computation time of a gate is directly linked to the charge et de discharge times.


is the NMOS transistor an efficient switch ?

 NMOS transistor discharging a capacitor C_u



is the NMOS transistor an efficient switch ?


NMOS transistor charging a capacitor C_u

 

NMOS versus PMOS

Equal geometries transistors

$$I_{DSN} - I_{DSP}$$

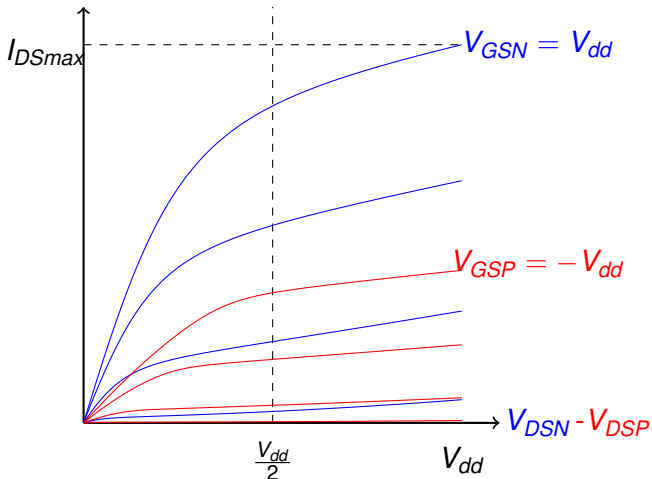

NMOS versus PMOS

- NMOS drain-source current is a electron current.
- PMOS drain-source current is a hole current.
- Charge mobility are different because componants are different
- With identical geometries and identical voltages (V_{gs} , V_{ds}), I_{ds} currents are different.
- PMOS transistor is less efficient than NMOS transistor

Stacked switches : body effect

- Threshold voltage value is linked to V_{sb} voltage

switches efficiency ?

A few common-sense rules

- NMOS preferred usage is discharging capacitors (generation of logic zeros)
- PMOS preferred usage is charging capacitors. (generation of logic ones)
- For equal efficiency, PMOS transistors should have larger width than NMOS transistors.
- Transistors stacks should be limited to 3 or 4 transistors.

Performance criterions

■ **Area/cost :**

The smaller the chip is, the better the efficiency of production and therefore the lower the manufacturing cost.

- Using smaller transistors (technology evolution)
- Using less transistors (architectural choices)

■ **Speed :**

Faster logic gates implies larger processing power.

- How to increase the clock frequency ?

■ **-> Power consumption :**


Computation means power consumption.

- How to minimize this power consumption ? (Internet Of Things) ...)
- How to evacuate the dissipated heat (Servers for cloud). . .)

Computation time of a logic gate


The simple case of a rising edge at the input of an inverter

 - Hypothesis 1 : The rising edge has a null duration.
- Hypothesis 2 : The only parasitic capacitance taken into account is the gate capacitance.
- Hypothesis 3 : The current flowing through the transistors for charge or discharge of parasitic capacitance C_{par} is roughly equal to I_{DSmax}



Computation time of a logic gate

MOS transistor

 

Current through the conducting transistor

$$I_{DS_{max}} = K_n \cdot (V_{dd} - V_{TN})^2 \text{ with } K_n = \frac{1}{2} \mu_{0N} \cdot C'_{ox} \frac{W_N}{L_N}$$

Parasitic capacitance of the transistor gate

$$C_{ox} = C'_{ox} W_N \cdot L_N$$

Computation time of a logic gate

Computation time of an invertor

Current equation for the parasitic capacitance

$$I_{C_{par}} = C_{par} dV_{C_{par}} / dt$$

The NMOS transistor acts as a current source

$$I_{C_{par}} \approx I_{DSmax} = K_n \cdot (V_{dd} - V_{tn})^2$$


Discharge from V_{dd} to 0

$$t_{comp} = C_{par} \frac{\Delta V}{I_{DSmax}} = C_{par} \frac{V_{dd}}{K_n \cdot (V_{dd} - V_{tn})^2}$$


Increasing the power-supply voltage in order to increase speed (overclocking) ? (bad way)

Power consumption of CMOS logic

Dissipated energy versus stored energy

 

Rising edge

 

Falling edge

Power consumption of CMOS logic

Energy balance

Charging : Energy comes from the power supply

$$E_{V_{dd}} = C_{par} \int_0^{V_{dd}} V_{dd} dV_s = C_{par} V_{dd}^2$$

Discharging : Stored energy in the capacitance

$$E_{C_{par}} = C_{par} \int_0^{V_{dd}} V_s dV_s = C_{par} \frac{V_{dd}^2}{2}$$

$C_{par} \frac{V_{dd}^2}{2}$ dissipation whatever the edge

Power consumption of CMOS logic

Power consumption of a full chip

- Let C_{chip} be the overall parasitic capacitance of the chip.
- Let F_{clk} be the operating frequency of the chip clock (synchronous logic)
- Let T_{act} (activity) be the mean transition probability of signals during a single cycle of the clock ($T_{act} \approx 0.3$)

Overall power consumption of the chip

$$P_{circuit} \approx T_{act} F_{clk} C_{chip} V_{dd}^2$$

What do you think now of overclocking ?

A bit of history

Moore's "law(s)"




Intel 1969 - 106 employees (2015 - 80000 employees)

https://commons.wikimedia.org/wiki/File:Intel_Mountain_View_in_1969.jpg

A bit of history

Moore's "law(s)"

 

- Gordon Moore, cofounder of Intel.
- Gordon Moore "Cramming More Components onto Integrated Circuits," Electronics, pp. 114–117, April 19, 1965.
- 1965 : « The complexity for minimum component costs has increased at a rate of roughly a factor of two per year »

<http://www.cs.utexas.edu/~fussell/courses/cs352h/papers/moore.pdf>

<http://www.intel.com/content/www/us/en/history/museum-gordon-moore-law.html>

A bit of history

Moore's "law(s)"

- This empirical observation became a prediction.
- This prediction became a roadmap for silicon foundries.
 - Research and development expenditure adjustment...
 - Investments expenditure adjustment for foundries...
 - ... in order to follow the roadmap.
- Moore'law widened to other key parameters :
 - Processing power of ... double every ... years
 - Power consumption of ... is divided by two every ... years

Moore's laws were exponential laws, followed during more than four decades.

Technology evolution model

"Theoretical downsizing"

■ Technology "nodes" :

- A technology node is defined by the minimum gate length of the transistor (90nm, 65nm, 40nm, 28nm, ...)
- For each new node silicon founders try to reduce the transistor area with a factor of **2**
- *Foundries* are investing billions of dollars in order to follow this objective ...

■ A linear reduction factor of $\beta = \sqrt{2}$ is used :

- The width W and the length L of transistors are divided by β .
- The oxide thickness T_{OX} is divided by β .
- The power supply voltage V_{dd} is divided by β .
- The threshold voltage V_T of the transistor is divided by β .

Theoretical downsizing

Performance evolutions

Parasitic capacitances as a function of β

$$C_{par}(\beta) = (W/\beta)(L/\beta)(\beta C'_{ox}) = \frac{C_{par}}{\beta}$$

Energy consumption of a gate as a function of β

$$E_{gate}(\beta) = \frac{C_{par}}{\beta} \left(\frac{V_{dd}}{\beta} \right)^2 = \frac{E_{gate}}{\beta^3}$$

Computation time of a gate as a function of β

$$t_{comp}(\beta) = \frac{t_{comp}}{\beta}$$

Theoretical downsizing

Reducing costs and power consumption

- Keeping the clock frequency constant.
 - $F_{clk}(\beta) = F_{clk}$
- The area reduction implies a price reduction
 - $Area(\beta) = \frac{Area}{\beta^2}$
- Power consumption is lower.
 - $P_{chip}(\beta) = T_{act} F_{clk} \frac{E_{chip}}{\beta^3} = \frac{P_{chip}}{\beta^3}$
- This strategy is particularly interesting for mobile systems :
 - Transition from high-end devices to low-end devices (smartphones),
 - New usages for ultra-low power devices (Internet Of Things).

Theoretical downsizing

Enhancing computational power


- Using maximum achievable frequency
 - $F_{clk}(\beta) = \beta F_{clk}$
- Using maximum achievable complexity (more transistors with the same area)
 - $Area(\beta) = Area$
- Power consumption doesn't change
 - $P_{chip}(\beta) = P_{chip}$
- This strategy is usefull for server CPUs.
 - Computational power is enhanced using higher frequencies.
 - Computational power is enhanced using parallelism.

MOS Transistor : 2004




PPC970fx (90nm)

MOS Transistor : 2008

 


Power6 (65nm)

MOS Transistor : 2011

 

Power7 (45nm)

MOS Transistor : 2013

 


Power7+ (32nm)


Using the same scale



2004
90nm
PPC970fx

 

2009
65nm
Power6

 

2011
45nm
Power7



2013
32 nm
Power7+



Photo Credits

The images are from the analysis of the evolution of IBM technologies made by Chipworks Inc.

The analysis as well as the original images were available in 2014 here :

<http://www.chipworks.com/en/technical-competitive-analysis/resources/blog/ibm-continues-major-source-chip-innovation/>

Practical downsizing

What are today problems ?


- For CPU, frequencies have reached their maximal values (from 3 to 4 GHz) at the beginning of the century. This is due to the maximum heat dissipation of the chips.
- When lowering the power-supply voltage we can no longer reach the "ideal switch" approximation : chips have larger and larger static dissipation added to the computation dissipation.
- Technologists must use more and more complex (costly) manufacturing processes to continue to follow the "Moore's Law"..
- At the end of the previous century, some predicted the end for "Moore's law" for scientific reasons (MOS transistor physics), it seems, since 2014, that the main difficulty is economical.

Technology downsizing

(forecast 2013) The end of Moore's law ?

Shrinking chips

 
Number and length of transistors bought per \$



Technology downsizing

(forecast 2016) Controversy continues

Gate Cost Trend

 


Source: International Business Strategies, Inc.

Technology downsizing

(2016) TSMC technologies

TSMC Cell Cost Trend

 

ICK *KNOWLEDGE LLC*


Source: IC Knowledge LLC –
Strategic Cost Model – 2016 – revision 07

3

Technology downsizing

(2017) Intel Investor Meeting

COST PER TRANSISTOR

 


**ALTHOUGH WAFER COST IS GOING UP,
COST PER TRANSISTOR CONTINUES TO DECLINE**

intel INVESTOR MEETING
FEBRUARY 2017 | 13

Forecasts are Intel estimates, based upon current expectations and available information and are subject to change without notice.

Technology downsizing

 
(2017) Gate length is no longer a good metric



Technology downsizing

Concept of "Standard node"

 
$$\text{Cell_area} \propto CPP * MMP * \text{Tracks}$$



Technology downsizing

"Standard Node Versus area formula"

 
- source : <https://www.semiwiki.com>
- 54 processes from 12 companies




Technology downsizing

"Standard Node By Company"

 - source : <https://www.semiwiki.com>
- Annoucements : Intel(14nm, 10nm) Tsmc(16nm, 10nm, 7nm)



 

Gordon Moore Fishing



source https://commons.wikimedia.org/wiki/File:Gordon_moore_fishing.jpg