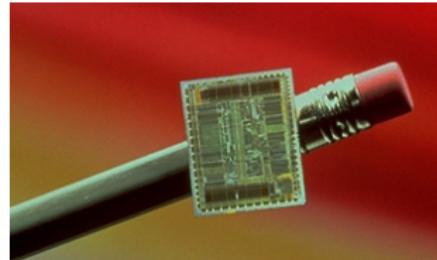




INSTITUT
Mines-Télécom



ICS904/EN2 : Design of Digital Integrated Circuits

L3 : Structural design of digital
circuits(2/2)

Yves MATHIEU

yves.mathieu@telecom-paristech.fr





Outline

Dynamic logic

Differential logic

Application specific logic

Performance optimization


Sequential cells

Standard cell design

Practical work

From NMOS logic to dynamic logic


pseudo-NMOS logic

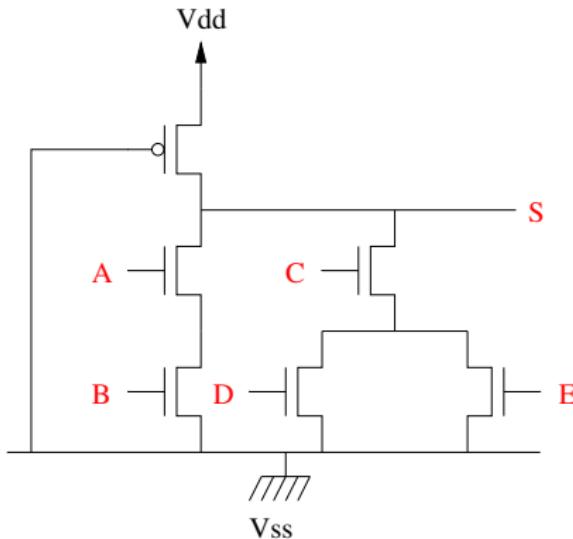

- Replacement of the PMOS network by a passive load.
- Smaller : The "1" values of the truth table are implicit values.
- CONFLICT : When NMOS network is ON : steady-state current.

From NMOS logic to dynamic logic


pseudo-NMOS logic

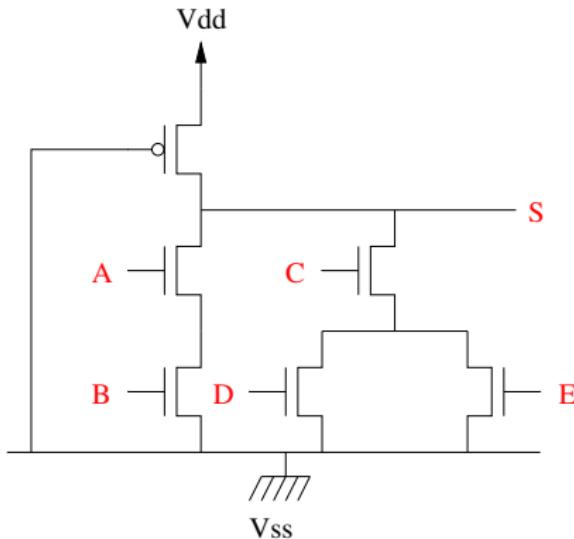

- Replacement of the PMOS network by a passive load.
- Smaller : The "1" values of the truth table are implicit values.
- CONFLICT : When NMOS network is ON : steady-state current.

From NMOS logic to dynamic logic


pseudo-NMOS logic

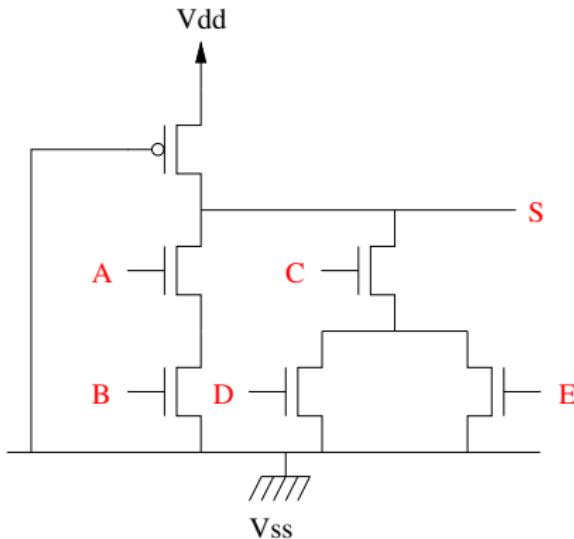

- Replacement of the PMOS network by a passive load.
- Smaller : The "1" values of the truth table are implicit values.
- CONFLICT : When NMOS network is ON : steady-state current.

From NMOS logic to Dynamic logic

pseudo NMOS-logic

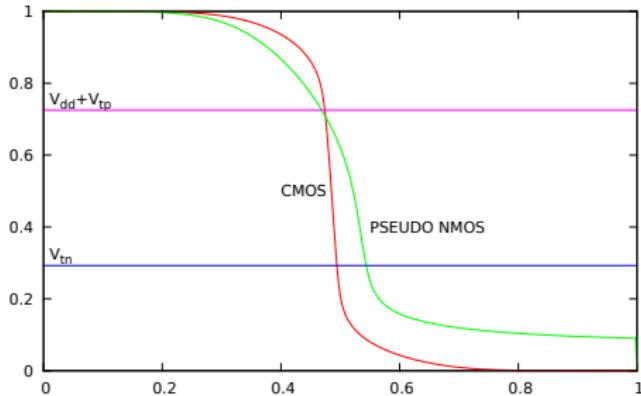


■ PMOS/NMOS width balancing :

- Low output level should be less than threshold voltage of NMOS transistor.
- Propagation time for output rising edge should be kept small.

■ How to avoid a choice between speed and low-power/robustness.

From NMOS logic to Dynamic logic

pseudo NMOS-logic

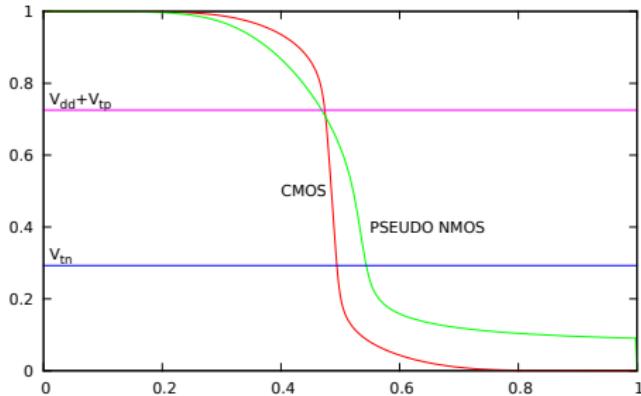


■ PMOS/NMOS width balancing :

- Low output level should be less than threshold voltage of NMOS transistor.
- Propagation time for output rising edge should be kept small.

■ How to avoid a choice between speed and low-power/robustness.

From NMOS logic to Dynamic logic

pseudo NMOS-logic

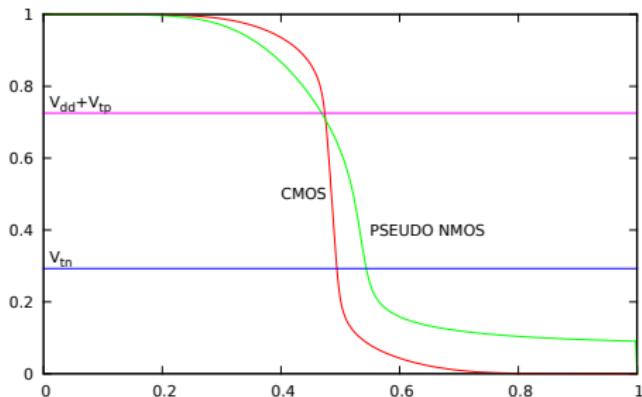


■ PMOS/NMOS width balancing :

- Low output level should be less than threshold voltage of NMOS transistor.
- Propagation time for output rising edge should be kept small.

■ How to avoid a choice between speed and low-power/robustness.

From NMOS logic to Dynamic logic

pseudo NMOS-logic

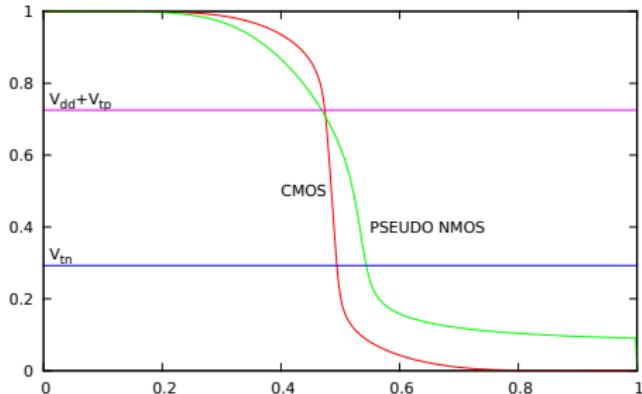


■ PMOS/NMOS width balancing :

- Low output level should be less than threshold voltage of NMOS transistor.
- Propagation time for output rising edge should be kept small.

■ How to avoid a choice between speed and low-power/robustness.

Dynamic logic


Precharge logic

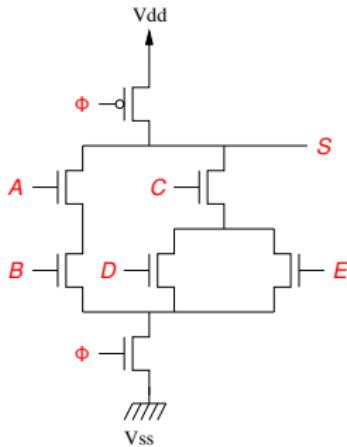

- Only one NMOS network.
- One clock (synchronous context)
- $\Phi = 0$: Output is precharged to 1 (Precharge phase)
- $\Phi = 1$: Conditional computation of the output. (Evaluation phase)
- State "1" is a high impedance state.
- Leakage current of transistors limits the minimum clock frequency (state "1" disappears ...).

Dynamic logic


Precharge logic

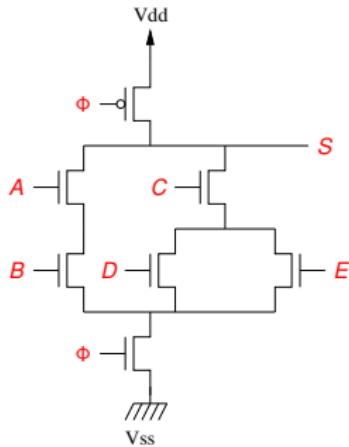


- Only one NMOS network.
- One clock (synchronous context)
 - $\Phi = 0$: Output is precharged to 1 (Precharge phase)
 - $\Phi = 1$: Conditional computation of the output. (Evaluation phase)
 - State "1" is a high impedance state.
 - Leakage current of transistors limits the minimum clock frequency (state "1" disappears ...).

Dynamic logic

Precharge logic

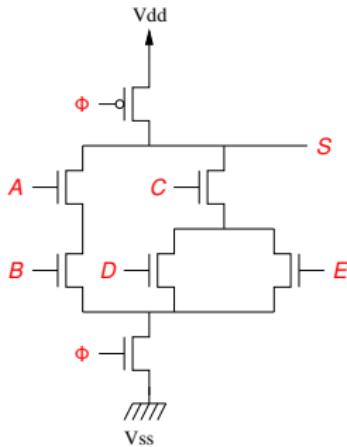

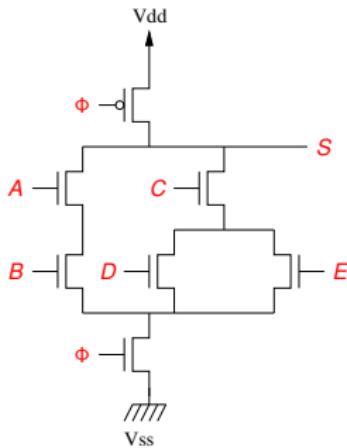
- Only one NMOS network.
- One clock (synchronous context)
- $\Phi = 0$: Output is precharged to 1 (Precharge phase)
- $\Phi = 1$: Conditional computation of the output. (Evaluation phase)
- State "1" is a high impedance state.
- Leakage current of transistors limits the minimum clock frequency (state "1" disappears ...).



- Only one NMOS network.
- One clock (synchronous context)
- $\Phi = 0$: Output is precharged to 1
(Precharge phase)
- $\Phi = 1$: Conditional computation of the output. (Evaluation phase)
- State "1" is a high impedance state.
- Leakage current of transistors limits the minimum clock frequency (state "1" disappears ...).

Dynamic logic


Precharge logic

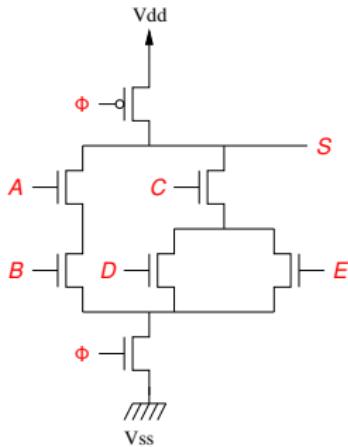

- Only one NMOS network.
- One clock (synchronous context)
- $\Phi = 0$: Output is precharged to 1 (Precharge phase)
- $\Phi = 1$: Conditional computation of the output. (Evaluation phase)
- State "1" is a high impedance state.
- Leakage current of transistors limits the minimum clock frequency (state "1" disappears . . .).

Dynamic logic

Precharge logic

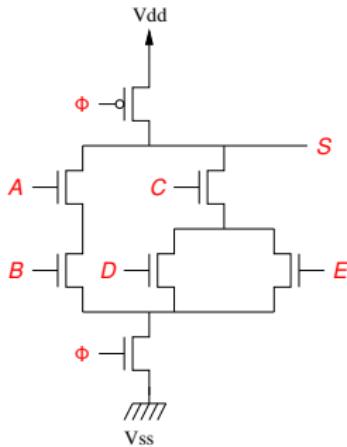

- Only one NMOS network.
- One clock (synchronous context)
- $\Phi = 0$: Output is precharged to 1 (Precharge phase)
- $\Phi = 1$: Conditional computation of the output. (Evaluation phase)
- State "1" is a high impedance state.
- Leakage current of transistors limits the minimum clock frequency (state "1" disappears ...).

- If the final state is "1", the output should stay to "1" during evaluation phase.
- So inputs should be stable during Evaluation phase.
- Then output of such cell can not be used as inputs of a another cell ...
- Even if we meet constraints, final output voltage may be less than V_{dd} (charge sharing inside the NMOS network)


- If the final state is "1", the output should stay to "1" during evaluation phase.
- So inputs should be stable during Evaluation phase.
- Then output of such cell can not be used as inputs of a another cell ...
- Even if we meet constraints, final output voltage may be less than V_{dd} (charge sharing inside the NMOS network)

- If the final state is "1", the output should stay to "1" during evaluation phase.
- So inputs should be stable during Evaluation phase.
- Then output of such cell can not be used as inputs of a another cell ...
- Even if we meet constraints, final output voltage may be less than V_{dd} (charge sharing inside the NMOS network)

- If the final state is "1", the output should stay to "1" during evaluation phase.
- So inputs should be stable during Evaluation phase.
- Then output of such cell can not be used as inputs of a another cell ...
- Even if we meet constraints, final output voltage may be less than V_{dd} (charge sharing inside the NMOS network)

Dynamic logic


Two phases dynamic logic

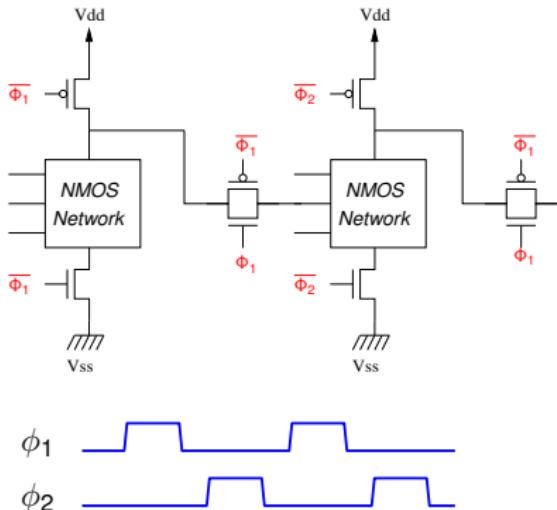

- Two clocks with non overlapping phases.
- Cell isolation using pass transistor logic and acting as a register.
- Fully cascadable, but odd and even cells should alternate
- Deep pipelining (no more than one gate level between each pipeline register)

Dynamic logic


Two phases dynamic logic

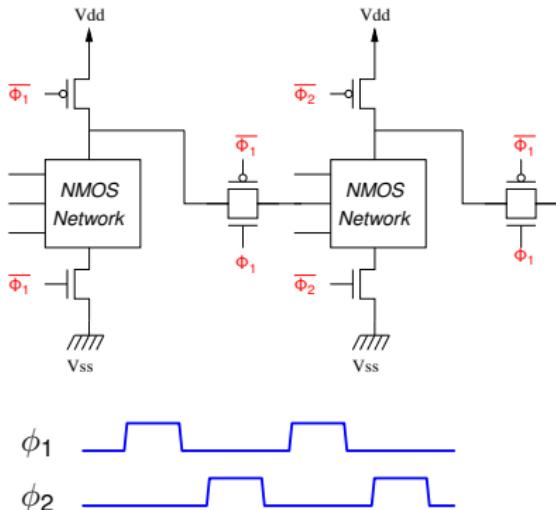

- Two clocks with non overlapping phases.
- Cell isolation using pass transistor logic and acting as a register.
- Fully cascadable, but odd and even cells should alternate
- Deep pipelining (no more than one gate level between each pipeline register)

Dynamic logic


Two phases dynamic logic

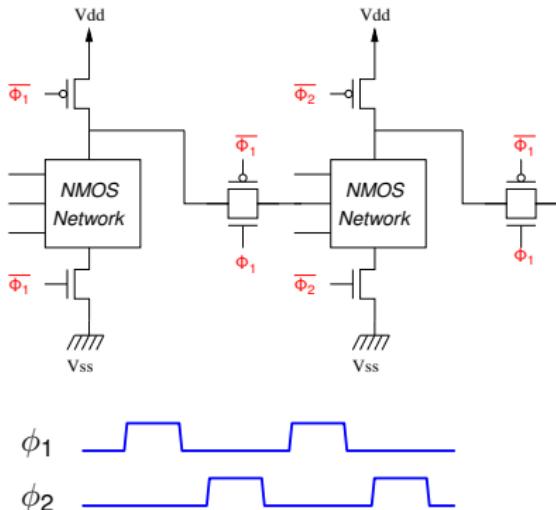


- Two clocks with non overlapping phases.
- Cell isolation using pass transistor logic and acting as a register.
- Fully cascadable, but odd and even cells should alternate
- Deep pipelining (no more than one gate level between each pipeline register)

Dynamic logic

Two phases dynamic logic

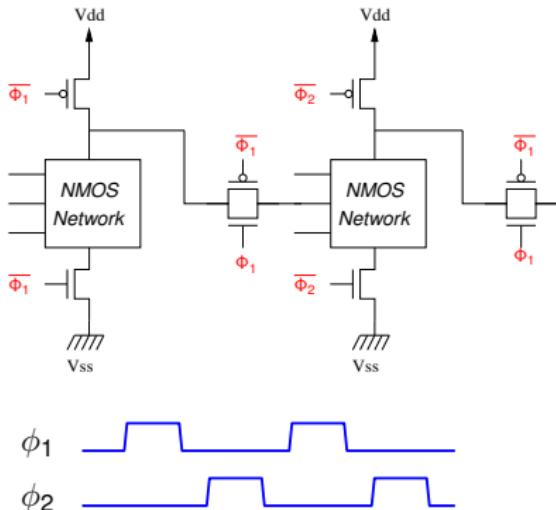

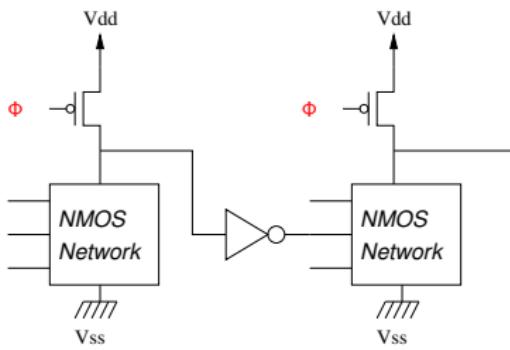- Two clocks with non overlapping phases.
- Cell isolation using pass transistor logic and acting as a register.
- Fully cascadable, but odd and even cells should alternate
- Deep pipelining (no more than one gate level between each pipeline register)




- During precharge phase : All gates inputs are "0" (all NMOS networks are OFF)
- During evaluation phase : some inputs switch to "1"
- Then some NMOS networks switch to ON state.
- Then some gate outputs switch to "0"
- Then some gate inputs switch to "1"
- ...
- $T_{cycle} > \sum T_{propagation}$

■ Warning : only non-inverting gate can be implemented


Dynamic logic

Domino logic

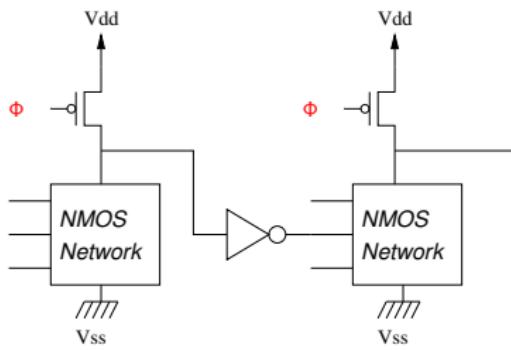


- During precharge phase : All gates inputs are "0" (all NMOS networks are OFF)
- During evaluation phase : some inputs switch to "1"
 - Then some NMOS networks switch to ON state.
 - Then some gate outputs switch to "0"
 - Then some gate inputs switch to "1"
 - ...
- $T_{cycle} > \sum T_{propagation}$

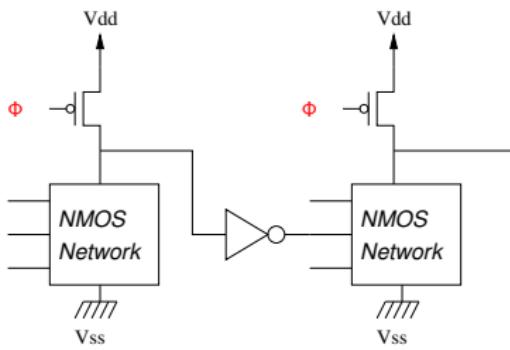- Warning : only non-inverting gate can be implemented



- During precharge phase : All gates inputs are "0" (all NMOS networks are OFF)
- During evaluation phase : some inputs switch to "1"
- Then some NMOS networks switch to ON state.
- Then some gate outputs switch to "0"
- Then some gate inputs switch to "1"
- ...
- $T_{cycle} > \sum T_{propagation}$

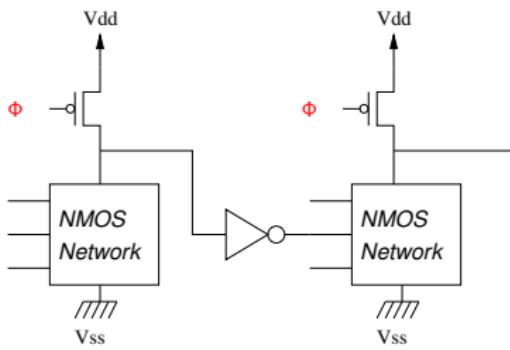■ Warning : only non-inverting gate can be implemented




- During precharge phase : All gates inputs are "0" (all NMOS networks are OFF)
- During evaluation phase : some inputs switch to "1"
- Then some NMOS networks switch to ON state.
- Then some gate outputs switch to "0"
- Then some gate inputs switch to "1"
...
- $T_{cycle} > \sum T_{propagation}$

■ Warning : only non-inverting gate can be implemented

Dynamic logic

Domino logic

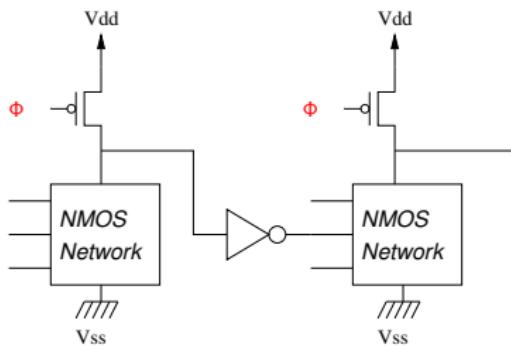


- During precharge phase : All gates inputs are "0" (all NMOS networks are OFF)
- During evaluation phase : some inputs switch to "1"
- Then some NMOS networks switch to ON state.
- Then some gate outputs switch to "0"
- Then some gate inputs switch to "1"
- ...
- $T_{cycle} > \sum T_{propagation}$

- Warning : only non-inverting gate can be implemented

Dynamic logic

Domino logic

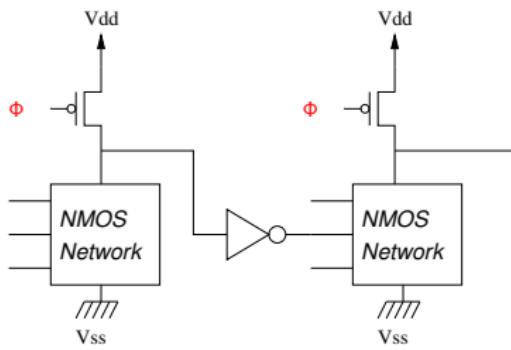


- During precharge phase : All gates inputs are "0" (all NMOS networks are OFF)
- During evaluation phase : some inputs switch to "1"
- Then some NMOS networks switch to ON state.
- Then some gate outputs switch to "0"
- Then some gate inputs switch to "1"
- ...
- $T_{cycle} > \sum T_{propagation}$

- Warning : only non-inverting gate can be implemented

Dynamic logic

Domino logic

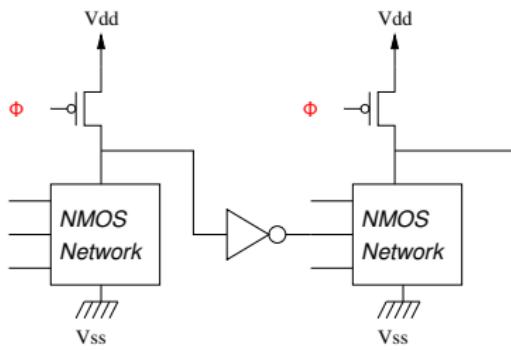


- During precharge phase : All gates inputs are "0" (all NMOS networks are OFF)
- During evaluation phase : some inputs switch to "1"
- Then some NMOS networks switch to ON state.
- Then some gate outputs switch to "0"
- Then some gate inputs switch to "1"
- ...
- $T_{cycle} > \sum T_{propagation}$

- Warning : only non-inverting gate can be implemented

Dynamic logic

Domino N-P logic

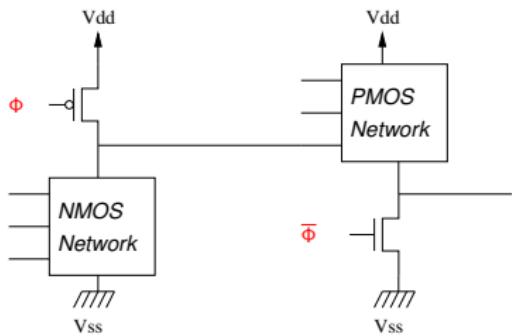

- Simplified : no more inverter
- Warning : only inverting gates can be implemented
- Warning : NMOS gates should alternate with PMOS gates...

- Very high speed logic (very small capacitive loads)
- Very often used during 80-90 years
- Example : High speed carry chain for arithmetic computation in microprocessors
- But : Clock is loaded by all cells... (power consumption of the clock network)
- But : Precharge phase is wasted time.
- But : Complex design automation (no direct RTL synthesis tool)
- Only used for optimized "full custom" designs.

- Very high speed logic (very small capacitive loads)
- Very often used during 80-90 years
- Example : High speed carry chain for arithmetic computation in microprocessors
- But : Clock is loaded by all cells... (power consumption of the clock network)
- But : Precharge phase is wasted time.
- But : Complex design automation (no direct RTL synthesis tool)
- Only used for optimized "full custom" designs.

- Very high speed logic (very small capacitive loads)
- Very often used during 80-90 years
- Example : High speed carry chain for arithmetic computation in microprocessors
- But : Clock is loaded by all cells... (power consumption of the clock network)
- But : Precharge phase is wasted time.
- But : Complex design automation (no direct RTL synthesis tool)
- Only used for optimized "full custom" designs.

- Very high speed logic (very small capacitive loads)
- Very often used during 80-90 years
- Example : High speed carry chain for arithmetic computation in microprocessors
- But : Clock is loaded by all cells... (power consumption of the clock network)
- But : Precharge phase is wasted time.
- But : Complex design automation (no direct RTL synthesis tool)
- Only used for optimized "full custom" designs.

- Very high speed logic (very small capacitive loads)
- Very often used during 80-90 years
- Example : High speed carry chain for arithmetic computation in microprocessors
- But : Clock is loaded by all cells... (power consumption of the clock network)
- But : Precharge phase is wasted time.
- But : Complex design automation (no direct RTL synthesis tool)
- Only used for optimized "full custom" designs.

- Very high speed logic (very small capacitive loads)
- Very often used during 80-90 years
- Example : High speed carry chain for arithmetic computation in microprocessors
- But : Clock is loaded by all cells... (power consumption of the clock network)
- But : Precharge phase is wasted time.
- But : Complex design automation (no direct RTL synthesis tool)
- Only used for optimized "full custom" designs.



Outline

Dynamic logic

Differential logic

Application specific logic

Performance optimization

Sequential cells

Standard cell design

Practical work

- All signals are duplicated : $A \Rightarrow (A_T, A_F)$
- Parallel computation of F and \bar{F}
- No invertor needed
- Reduces complexity of arithmetic computation.
- 2 NMOS transistors networks of equal size.
- No limitation to inverting or non inverting gates.
- Less number of gates, but more wires . . .

- All signals are duplicated : $A \Rightarrow (A_T, A_F)$
- Parallel computation of F and \bar{F}
- No invertor needed
- Reduces complexity of arithmetic computation.
- 2 NMOS transistors networks of equal size.
- No limitation to inverting or non inverting gates.
- Less number of gates, but more wires ...

Introduction

- All signals are duplicated : $A \Rightarrow (A_T, A_F)$
- Parallel computation of F and \bar{F}
- No invertor needed
- Reduces complexity of arithmetic computation.
- 2 NMOS transistors networks of equal size.
- No limitation to inverting or non inverting gates.
- Less number of gates, but more wires . . .

Introduction

- All signals are duplicated : $A \Rightarrow (A_T, A_F)$
- Parallel computation of F and \bar{F}
- No invertor needed
- Reduces complexity of arithmetic computation.
- 2 NMOS transistors networks of equal size.
- No limitation to inverting or non inverting gates.
- Less number of gates, but more wires ...

Introduction

- All signals are duplicated : $A \Rightarrow (A_T, A_F)$
- Parallel computation of F and \bar{F}
- No invertor needed
- Reduces complexity of arithmetic computation.
- 2 NMOS transistors networks of equal size.
- No limitation to inverting or non inverting gates.
- Less number of gates, but more wires . . .

Introduction


- All signals are duplicated : $A \Rightarrow (A_T, A_F)$
- Parallel computation of F and \bar{F}
- No invertor needed
- Reduces complexity of arithmetic computation.
- 2 NMOS transistors networks of equal size.
- No limitation to inverting or non inverting gates.
- Less number of gates, but more wires . . .

Introduction

- All signals are duplicated : $A \Rightarrow (A_T, A_F)$
- Parallel computation of F and \bar{F}
- No invertor needed
- Reduces complexity of arithmetic computation.
- 2 NMOS transistors networks of equal size.
- No limitation to inverting or non inverting gates.
- Less number of gates, but more wires . . .

Differential logic


Cascode Voltage Switch Logic

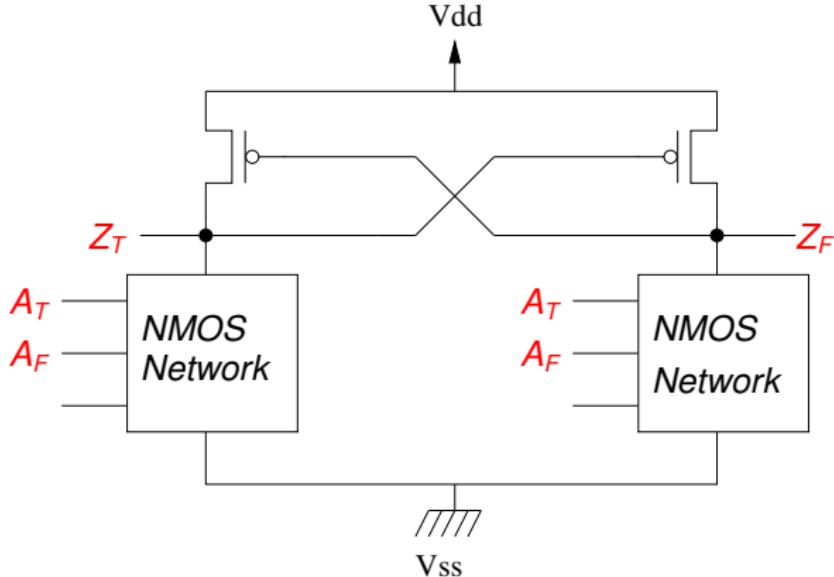

- Warning : conflicts during output transitions.
- Slower than CMOS logic.
- The two networks can share transistors

Differential logic


Cascode Voltage Switch Logic

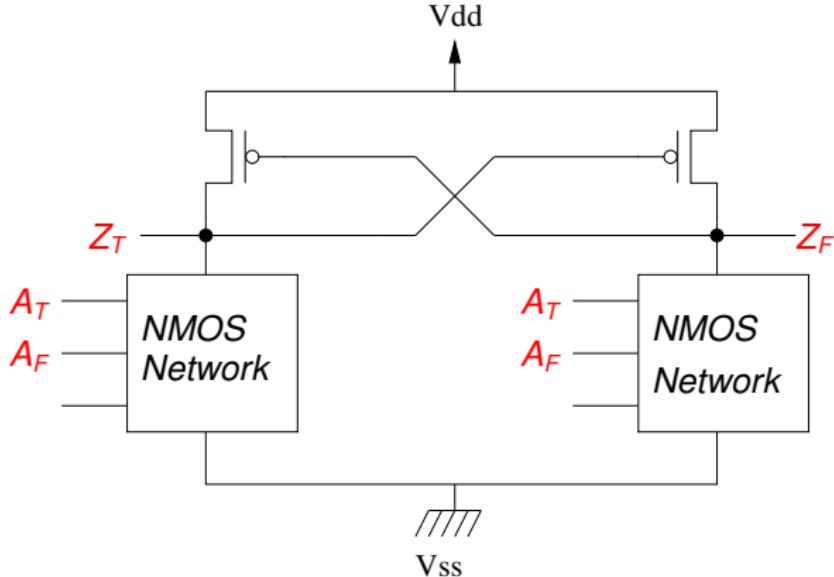

- Warning : conflicts during output transitions.
- Slower than CMOS logic.
- The two networks can share transistors

Differential logic


Cascode Voltage Switch Logic

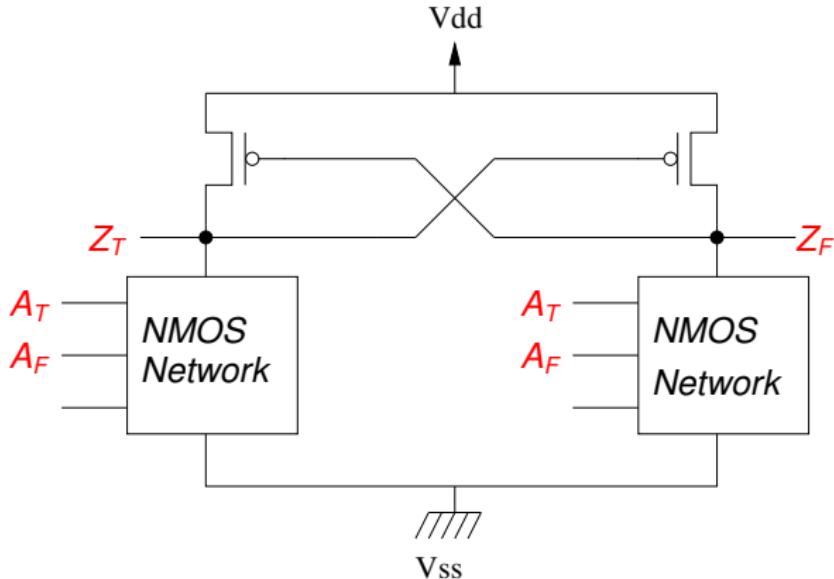

- Warning : conflicts during output transitions.
- Slower than CMOS logic.
- The two networks can share transistors

Differential logic

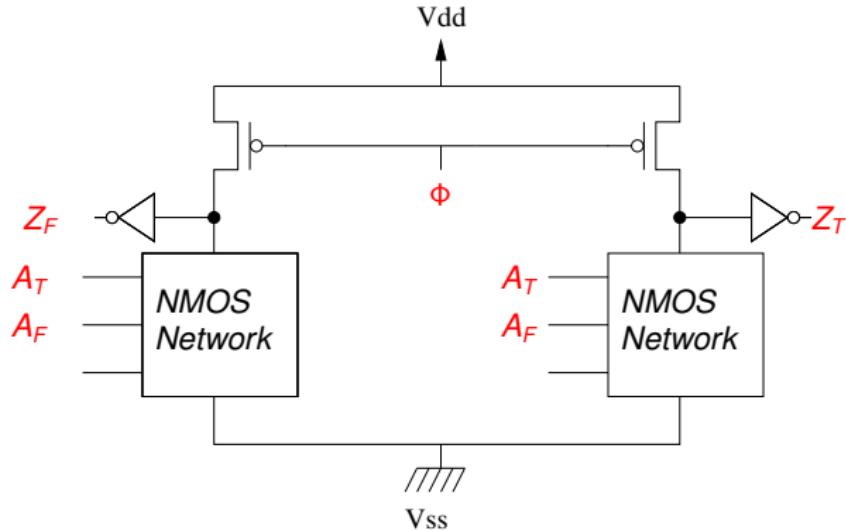
DCVSL : Dynamic Cascode Voltage Switch Logic



- No conflict during output transitions.
- Q1 : Design a CVSL 2 inputs XOR gate. Try to minimize the number of transistors.

Differential logic

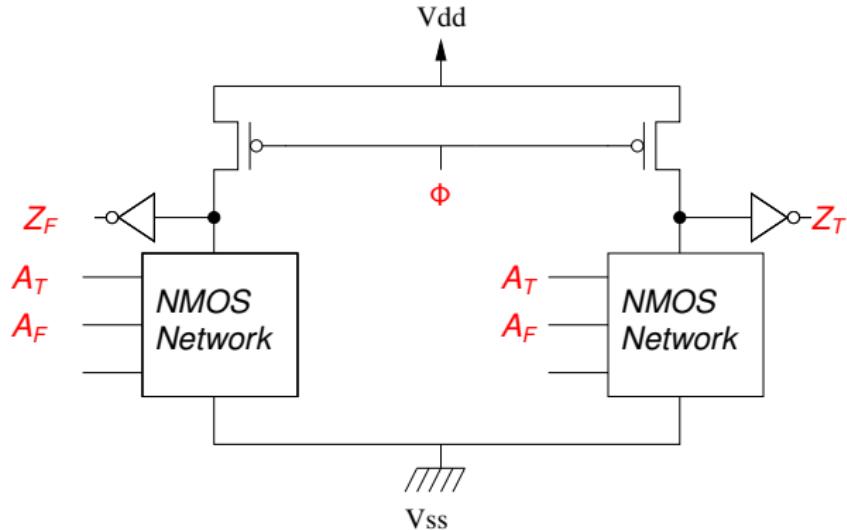
DCVSL : Dynamic Cascode Voltage Switch Logic



- No conflict during output transitions.
- **Q1** : Design a CVSL 2 inputs XOR gate. Try to minimize the number of transistors.

Differential logic


CPL : Complementary Pass Logic

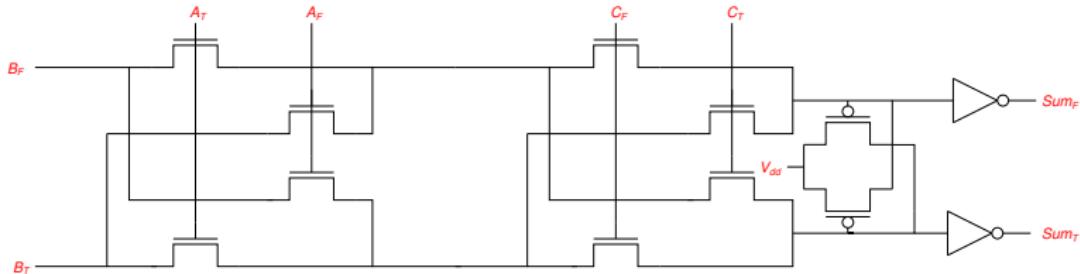

- Pass transistor logic using only NMOS : slow degraded logic one but ...
- "Weak" PMOS pullups restore full scale swing and outputs are buffered by CMOS invertors
- Using *low* V_t transistor for the network, and *high* V_t transistors for the invertors helps speed optimization
- Said to be one of the fastest logic style ...

Differential logic


CPL : Complementary Pass Logic

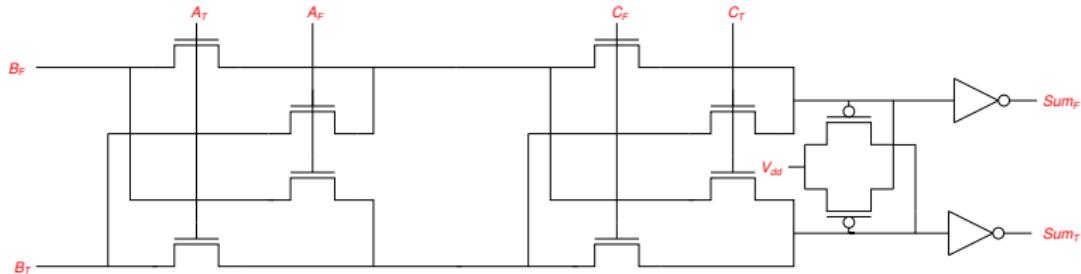

- Pass transistor logic using only NMOS : slow degraded logic one but ...
- "Weak" PMOS pullups restore full scale swing and outputs are buffered by CMOS invertors
- Using *low* V_t transistor for the network, and *high* V_t transistors for the invertors helps speed optimization
- Said to be one of the fastest logic style ...

Differential logic


CPL : Complementary Pass Logic

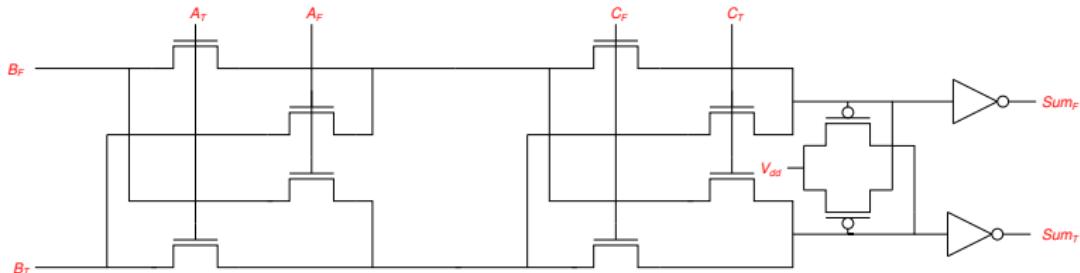

- Pass transistor logic using only NMOS : slow degraded logic one but ...
- "Weak" PMOS pullups restore full scale swing and outputs are buffered by CMOS invertors
- Using *low* V_t transistor for the network, and *high* V_t transistors for the invertors helps speed optimization
- Said to be one of the fastest logic style ...

Differential logic

CPL : Complementary Pass Logic

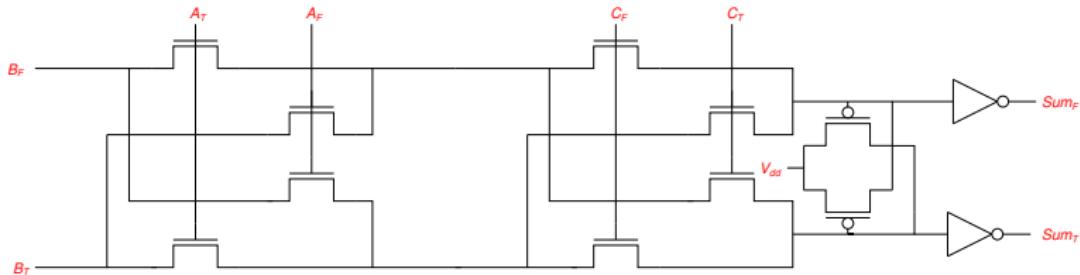

- Pass transistor logic using only NMOS : slow degraded logic one but ...
- "Weak" PMOS pullups restore full scale swing and outputs are buffered by CMOS invertors
- Using *low* V_t transistor for the network, and *high* V_t transistors for the invertors helps speed optimization
- Said to be one of the fastest logic style ...



Outline

Dynamic logic

Differential logic

Application specific logic

Performance optimization

Sequential cells

Standard cell design

Practical work



Differential logic

Application specific logic styles

- Current Mode Logics
- Adiabatic Logic
- SubThreshold Logic
- ...



Differential logic

Application specific logic styles

- Current Mode Logics
- Adiabatic Logic
- SubThreshold Logic
- ...



Differential logic

Application specific logic styles

- Current Mode Logics
- Adiabatic Logic
- SubThreshold Logic
- . . .



Differential logic

Application specific logic styles

- Current Mode Logics
- Adiabatic Logic
- SubThreshold Logic
- ...



Outline

Dynamic logic

Differential logic

Application specific logic

Performance optimization

Sequential cells

Standard cell design

Practical work

Introduction

- Area of the logic gates.
- Speed of the logic gates.
- Power consumption of the logic gates
- Noise margin of the logic gates
- EDP : "Energy Delay Product" of the logic gates.
- Near threshold or Sub-threshold behavior.
- Robustness of the design.
- ...



Performance metrics

Introduction

- Area of the logic gates.
- Speed of the logic gates.
- Power consumption of the logic gates
- Noise margin of the logic gates
- EDP : "Energy Delay Product" of the logic gates.
- Near threshold or Sub-threshold behavior.
- Robustness of the design.
- ...



Performance metrics

Introduction

- Area of the logic gates.
- Speed of the logic gates.
- Power consumption of the logic gates
- Noise margin of the logic gates
- EDP : "Energy Delay Product" of the logic gates.
- Near threshold or Sub-threshold behavior.
- Robustness of the design.
- ...



Performance metrics

Introduction

- Area of the logic gates.
- Speed of the logic gates.
- Power consumption of the logic gates
- Noise margin of the logic gates
- EDP : "Energy Delay Product" of the logic gates.
- Near threshold or Sub-threshold behavior.
- Robustness of the design.
- ...

Introduction

- Area of the logic gates.
- Speed of the logic gates.
- Power consumption of the logic gates
- Noise margin of the logic gates
- EDP : "Energy Delay Product" of the logic gates.
- Near threshold or Sub-threshold behavior.
- Robustness of the design.
- ...

Introduction

- Area of the logic gates.
- Speed of the logic gates.
- Power consumption of the logic gates
- Noise margin of the logic gates
- EDP : "Energy Delay Product" of the logic gates.
- Near threshold or Sub-threshold behavior.
- Robustness of the design.
- ...



Performance metrics

Introduction

- Area of the logic gates.
- Speed of the logic gates.
- Power consumption of the logic gates
- Noise margin of the logic gates
- EDP : "Energy Delay Product" of the logic gates.
- Near threshold or Sub-threshold behavior.
- Robustness of the design.
- . . .

Introduction

- Area of the logic gates.
- Speed of the logic gates.
- Power consumption of the logic gates
- Noise margin of the logic gates
- EDP : "Energy Delay Product" of the logic gates.
- Near threshold or Sub-threshold behavior.
- Robustness of the design.
- ...

Buffer optimization example

simple inverter

- Problem definition : What is the fastest way to transmit a data from the input of gate A, to the inputs of gates connected to A ?
- The timing model of gate A is known : $T_{pA} = T_{p0A} + R_A \cdot C_{load}$
- The inputs of the gates connected to A are modeled by a load capacitor C_{LdA}
- A parametrized inverter can be used :
 - $T_{pIV}(\alpha) = T_{p0IV} + (R_{0IV}/\alpha) \cdot C_{load}$
 - $C_{InIV}(\alpha) = C_{0InIV} \cdot \alpha$
 - with $\alpha \geq 1.0$
- The inverter is inserted between gate A and the other gates.
- Compute the propagation time through the gates α
- Compute the value of α giving the minimum propagation time.
- Compute the value of the minimum propagation time.

Buffer optimization example

simple inverter

- Problem definition : What is the fastest way to transmit a data from the input of gate A, to the inputs of gates connected to A ?
- The timing model of gate A is known : $T_{pA} = T_{p0A} + R_A \cdot C_{load}$
- The inputs of the gates connected to A are modeled by a load capacitor C_{LdA}
- A parametrized inverter can be used :
 - $T_{pIV}(\alpha) = T_{p0IV} + (R_{0IV}/\alpha) \cdot C_{load}$
 - $C_{InIV}(\alpha) = C_{0InIV} \cdot \alpha$
 - with $\alpha \geq 1.0$
- The inverter is inserted between gate A and the other gates.
- Compute the propagation time through the gates α
- Compute the value of α giving the minimum propagation time.
- Compute the value of the minimum propagation time.

Buffer optimization example

simple inverter

- Problem definition : What is the fastest way to transmit a data from the input of gate A, to the inputs of gates connected to A ?
- The timing model of gate A is known : $T_{pA} = T_{p0A} + R_A \cdot C_{load}$
- The inputs of the gates connected to A are modeled by a load capacitor C_{LdA}
- A parametrized inverter can be used :
 - $T_{pIV}(\alpha) = T_{p0IV} + (R_{0IV}/\alpha) \cdot C_{load}$
 - $C_{Inv}(\alpha) = C_{0Inv} \cdot \alpha$
 - with $\alpha \geq 1.0$
- The inverter is inserted between gate A and the other gates.
- Compute the propagation time through the gates α
- Compute the value of α giving the minimum propagation time.
- Compute the value of the minimum propagation time.

Buffer optimization example

simple inverter

- Problem definition : What is the fastest way to transmit a data from the input of gate A, to the inputs of gates connected to A ?
- The timing model of gate A is known : $T_{pA} = T_{p0A} + R_A \cdot C_{load}$
- The inputs of the gates connected to A are modeled by a load capacitor C_{LdA}
- A parametrized inverter can be used :
 - $T_{pIV}(\alpha) = T_{p0IV} + (R_{0IV}/\alpha) \cdot C_{load}$
 - $C_{InIV}(\alpha) = C_{0InIV} \cdot \alpha$
 - with $\alpha \geq 1.0$
- The inverter is inserted between gate A and the other gates.
- Compute the propagation time through the gates α
- Compute the value of α giving the minimum propagation time.
- Compute the value of the minimum propagation time.

Buffer optimization example

simple inverter

- Problem definition : What is the fastest way to transmit a data from the input of gate A, to the inputs of gates connected to A ?
- The timing model of gate A is known : $T_{pA} = T_{p0A} + R_A \cdot C_{load}$
- The inputs of the gates connected to A are modeled by a load capacitor C_{LdA}
- A parametrized inverter can be used :
 - $T_{pIV}(\alpha) = T_{p0IV} + (R_{0IV}/\alpha) \cdot C_{load}$
 - $C_{InIV}(\alpha) = C_{0InIV} \cdot \alpha$
 - with $\alpha \geq 1.0$
- The inverter is inserted between gate A and the other gates.
- Compute the propagation time through the gates α
- Compute the value of α giving the minimum propagation time.
- Compute the value of the minimum propagation time.

Buffer optimization example

simple inverter

- Problem definition : What is the fastest way to transmit a data from the input of gate A, to the inputs of gates connected to A ?
- The timing model of gate A is known : $T_{pA} = T_{p0A} + R_A \cdot C_{load}$
- The inputs of the gates connected to A are modeled by a load capacitor C_{LdA}
- A parametrized inverter can be used :
 - $T_{pIV}(\alpha) = T_{p0IV} + (R_{0IV}/\alpha) \cdot C_{load}$
 - $C_{InIV}(\alpha) = C_{0InIV} \cdot \alpha$
 - with $\alpha \geq 1.0$
- The inverter is inserted between gate A and the other gates.
- Compute the propagation time through the gates α
- Compute the value of α giving the minimum propagation time.
- Compute the value of the minimum propagation time.

Buffer optimization example

simple inverter

- Problem definition : What is the fastest way to transmit a data from the input of gate A, to the inputs of gates connected to A ?
- The timing model of gate A is known : $T_{pA} = T_{p0A} + R_A \cdot C_{load}$
- The inputs of the gates connected to A are modeled by a load capacitor C_{LdA}
- A parametrized inverter can be used :
 - $T_{pIV}(\alpha) = T_{p0IV} + (R_{0IV}/\alpha) \cdot C_{load}$
 - $C_{InIV}(\alpha) = C_{0InIV} \cdot \alpha$
 - with $\alpha \geq 1.0$
- The inverter is inserted between gate A and the other gates.
- Compute the propagation time through the gates α
- Compute the value of α giving the minimum propagation time.
- Compute the value of the minimum propagation time.



Buffer optimization example

several invertors

- The invertor is replaced by two successive invertors with parameters α_0 and α_1 .
- What are the optimal sizes of α_0 and α_1 for a minimum propagation time ?
- Compute the value of the minimum propagation time.
- The two invertors are replaced by N successive invertors with parameters $\alpha_0 \dots \alpha_{N-1}$.
- What are the optimal sizes of the N parameters α_i for a minimum propagation time ?
- Compute the value of the minimum propagation time.
- Compute the value of N that minimize the propagation time
- Compute the value of the minimum propagation time.



Buffer optimization example

several invertors

- The invertor is replaced by two successive invertors with parameters α_0 and α_1 .
- What are the optimal sizes of α_0 and α_1 for a minimum propagation time ?
- Compute the value of the minimum propagation time.
- The two invertors are replaced by N successive invertors with parameters $\alpha_0 \dots \alpha_{N-1}$.
- What are the optimal sizes of the N parameters α_i for a minimum propagation time ?
- Compute the value of the minimum propagation time.
- Compute the value of N that minimize the propagation time
- Compute the value of the minimum propagation time.



Buffer optimization example

several invertors

- The invertor is replaced by two successive invertors with parameters α_0 and α_1 .
- What are the optimal sizes of α_0 and α_1 for a minimum propagation time ?
- Compute the value of the minimum propagation time.
- The two invertors are replaced by N successive invertors with parameters $\alpha_0 \dots \alpha_{N-1}$.
- What are the optimal sizes of the N parameters α_i for a minimum propagation time ?
- Compute the value of the minimum propagation time.
- Compute the value of N that minimize the propagation time
- Compute the value of the minimum propagation time.



Buffer optimization example

several invertors

- The invertor is replaced by two successive invertors with parameters α_0 and α_1 .
- What are the optimal sizes of α_0 and α_1 for a minimum propagation time ?
- Compute the value of the minimum propagation time.
- The two invertors are replaced by N successive invertors with parameters $\alpha_0 \dots \alpha_{N-1}$.
- What are the optimal sizes of the N parameters α_i for a minimum propagation time ?
- Compute the value of the minimum propagation time.
- Compute the value of N that minimize the propagation time
- Compute the value of the minimum propagation time.



Buffer optimization example

How to transmit a data on a long wire

- The long wire as a distributed RC model.
- Distributed inverters along the line may help minimizing overall propagation time.
- Same kind of optimization but with a non linear model of the propagation time through the line



Buffer optimization example

How to transmit a data on a long wire

- The long wire as a distributed RC model.
- Distributed inverters along the line may help minimizing overall propagation time.
- Same kind of optimization but with a non linear model of the propagation time through the line



Buffer optimization example

How to transmit a data on a long wire

- The long wire as a distributed RC model.
- Distributed invertors along the line may help minimizing overall propagation time.
- Same kind of optimization but with a non linear model of the propagation time through the line



Outline

Dynamic logic

Differential logic

Application specific logic

Performance optimization


Sequential cells

Standard cell design

Practical work

positive edge-triggered D flip-flop


Theoretical Master/Slave flip-flop

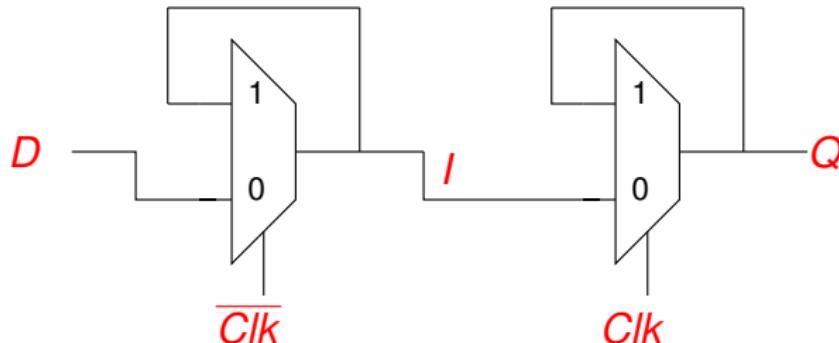

- Muxes with loops define 2 storage elements (Master and Slave)
- Master(resp. Slave) hold its value while Slave (resp. Master) is transparent.
- Skew between the two clocks should be avoided (race condition).
- D signal should respect timing conditions.
 - Setup time / Hold time

positive edge-triggered D flip-flop


Theoretical Master/Slave flip-flop

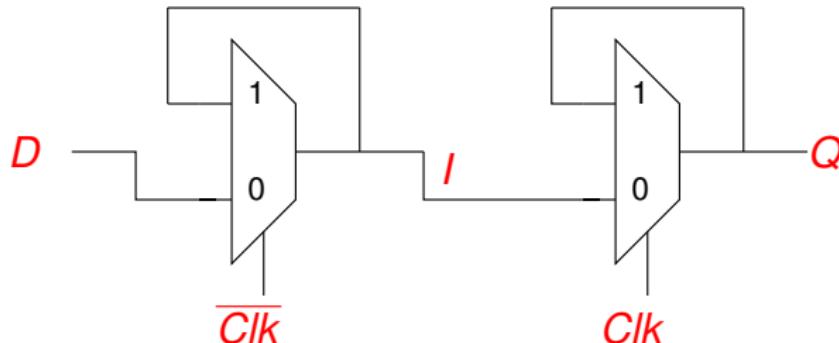

- Muxes with loops define 2 storage elements (Master and Slave)
- Master(resp. Slave) hold its value while Slave (resp. Master) is transparent.
- Skew between the two clocks should be avoided (race condition).
- D signal should respect timing conditions.
 - Setup time / Hold time

positive edge-triggered D flip-flop


Theoretical Master/Slave flip-flop

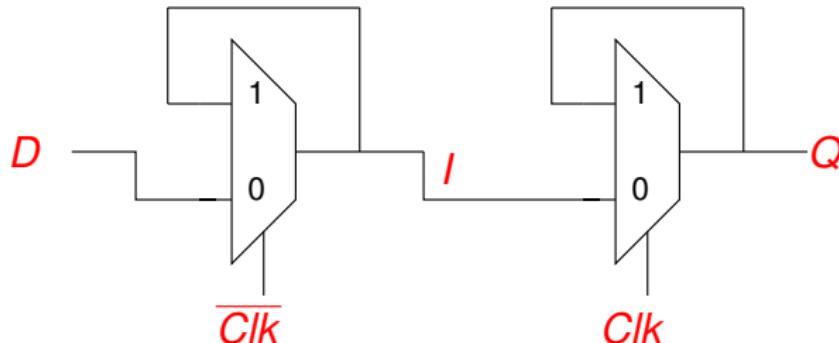

- Muxes with loops define 2 storage elements (Master and Slave)
- Master(resp. Slave) hold its value while Slave (resp. Master) is transparent.
- Skew between the two clocks should be avoided (race condition).
- D signal should respect timing conditions.
 - Setup time / Hold time


positive edge-triggered D flip-flop

Theoretical Master/Slave flip-flop

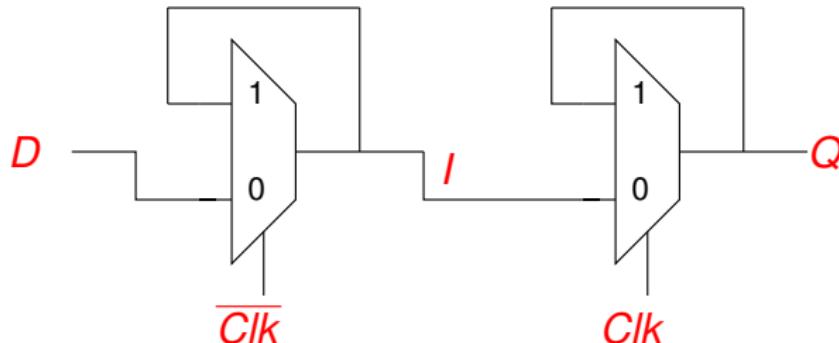


- Muxes with loops define 2 storage elements (Master and Slave)
- Master(resp. Slave) hold its value while Slave (resp. Master) is transparent.
- Skew between the two clocks should be avoided (race condition).
- D signal should respect timing conditions.
 - Setup time / Hold time

practical design

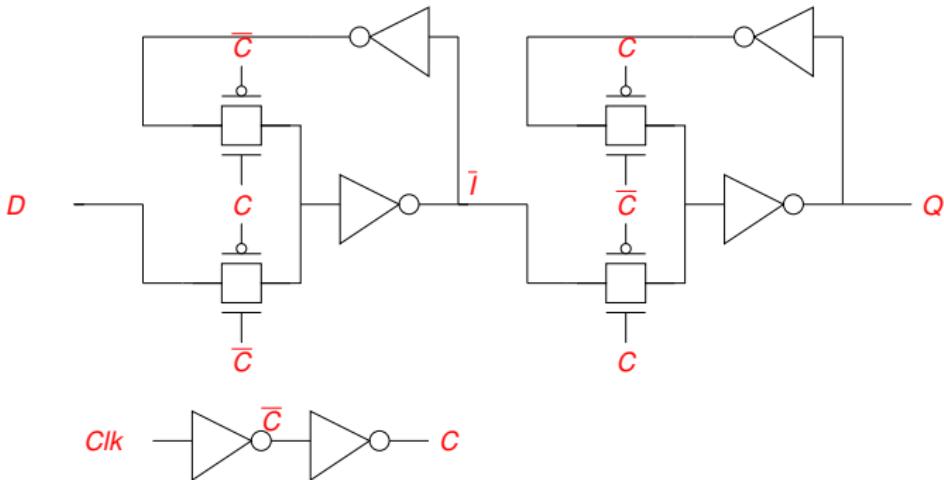


- Clocks are internally generated in order to avoid unwanted skew.
- Warning D input is on the Drain of a transistor
- One can mix CMOS logic and pass transistor logic (using tristate invertors).
- Q1 : Design a D flip/flop using tristate invertors

practical design

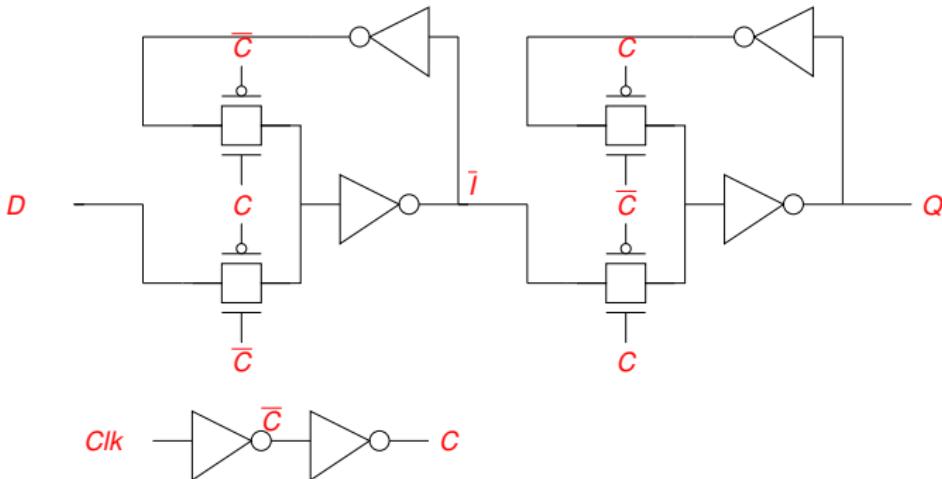


- Clocks are internally generated in order to avoid unwanted skew.
- Warning D input is on the Drain of a transistor
- One can mix CMOS logic and pass transistor logic (using tristate invertors).
- Q1 : Design a D flip/flop using tristate invertors

practical design

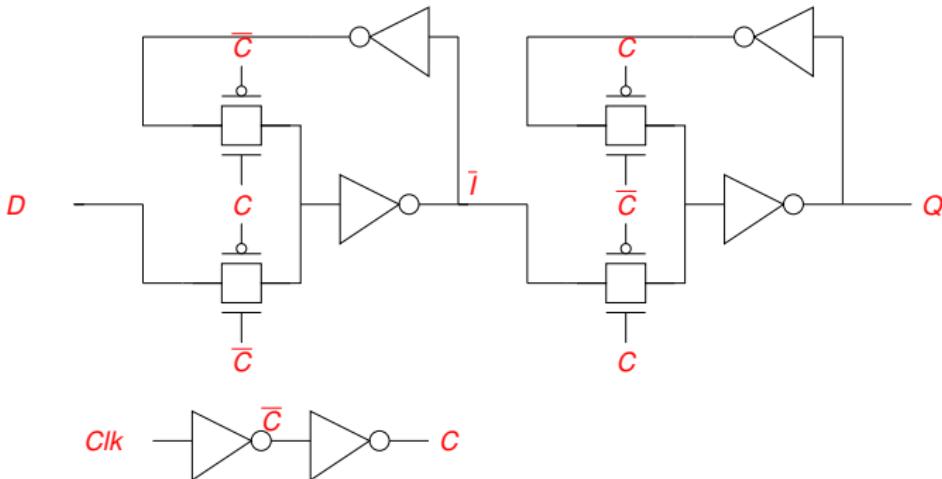

- Clocks are internally generated in order to avoid unwanted skew.
- Warning D input is on the Drain of a transistor
- One can mix CMOS logic and pass transistor logic (using tristate invertors).
- Q1 : Design a D flip/flop using tristate invertors

practical design

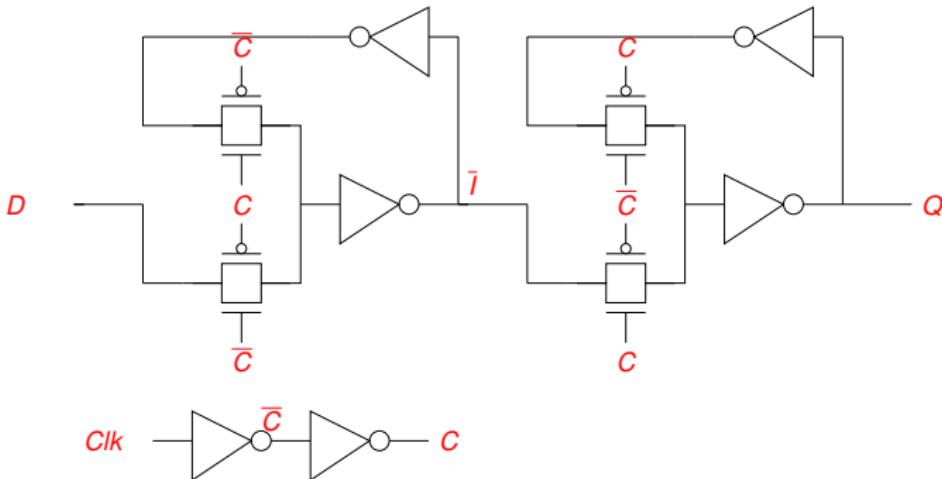

- Clocks are internally generated in order to avoid unwanted skew.
- Warning D input is on the Drain of a transistor
- One can mix CMOS logic and pass transistor logic (using tristate invertors).
- Q1 : Design a D flip/flop using tristate invertors



Outline

Dynamic logic

Differential logic

Application specific logic

Performance optimization

Sequential cells

Standard cell design

Practical work



"Standard Cells" versus "Full Custom"

Full Custom

- Manual layout of all needed cells.
- Long elec. simulations for verif. of a whole block.
- Wide logic styles choice.
- Scripting may help layout phases.
- Ultimate optimisation for speed power or area.
- Only for high value added digital or analog blocs.

Standard Cells

- Layout design limited to generic cells.
- Electrical simulation for cell properties extraction.
- Small logic styles choice.
- Automation of synthesis, place and route phases.
- Suboptimal for speed power and area.
- When time-to-market is the main criterion.



"Standard Cells" versus "Full Custom"

Full Custom

- Manual layout of all needed cells.
- Long elec. simulations for verif. of a whole block.
- Wide logic styles choice.
- Scripting may help layout phases.
- Ultimate optimisation for speed power or area.
- Only for high value added digital or analog blocs.

Standard Cells

- Layout design limited to generic cells.
- Electrical simulation for cell properties extraction.
- Small logic styles choice.
- Automation of synthesis, place and route phases.
- Suboptimal for speed power and area.
- When time-to-market is the main criterion.



"Standard Cells" versus "Full Custom"

Full Custom

- Manual layout of all needed cells.
- Long elec. simulations for verif. of a whole block.
- Wide logic styles choice.
- Scripting may help layout phases.
- Ultimate optimisation for speed power or area.
- Only for high value added digital or analog blocs.

Standard Cells

- Layout design limited to generic cells.
- Electrical simulation for cell properties extraction.
- Small logic styles choice.
- Automation of synthesis, place and route phases.
- Suboptimal for speed power and area.
- When time-to-market is the main criterion.

"Standard Cells" versus "Full Custom"


Full Custom

- Manual layout of all needed cells.
- Long elec. simulations for verif. of a whole block.
- Wide logic styles choice.
- Scripting may help layout phases.
- Ultimate optimisation for speed power or area.
- Only for high value added digital or analog blocs.

Standard Cells



- Layout design limited to generic cells.
- Electrical simulation for cell properties extraction.
- Small logic styles choice.
- Automation of synthesis, place and route phases.
- Suboptimal for speed power and area.
- When time-to-market is the main criterion.

Standard cell principles

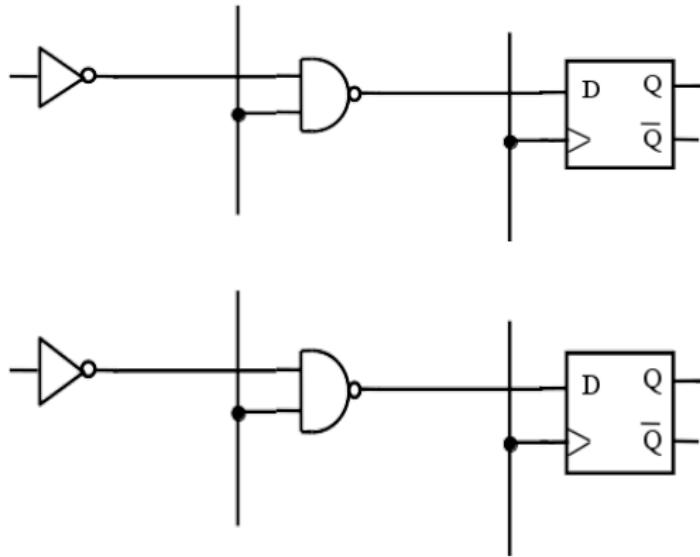


- All cells have same height
- Power supply and Ground connected by abutment.
- Cell design should be free of DRC error.
- Any abutment of any couple of cells should be free of DRC error.
- Wiring inside cell limited to Metal1 level.

Standard cell principles

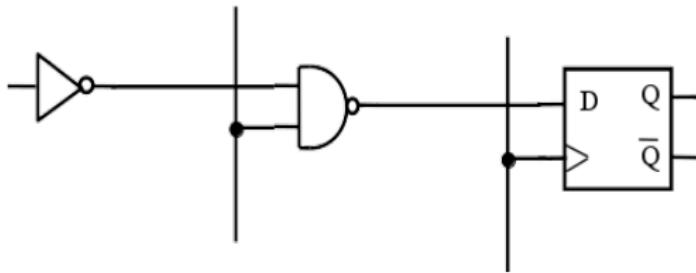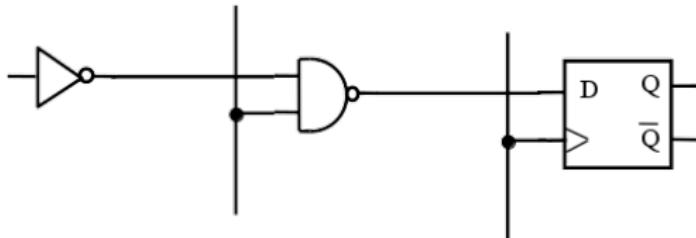


- All cells have same height
- Power supply and Ground connected by abutment.
- Cell design should be free of DRC error.
- Any abutment of any couple of cells should be free of DRC error.
- Wiring inside cell limited to Metal1 level.

Standard cell principles

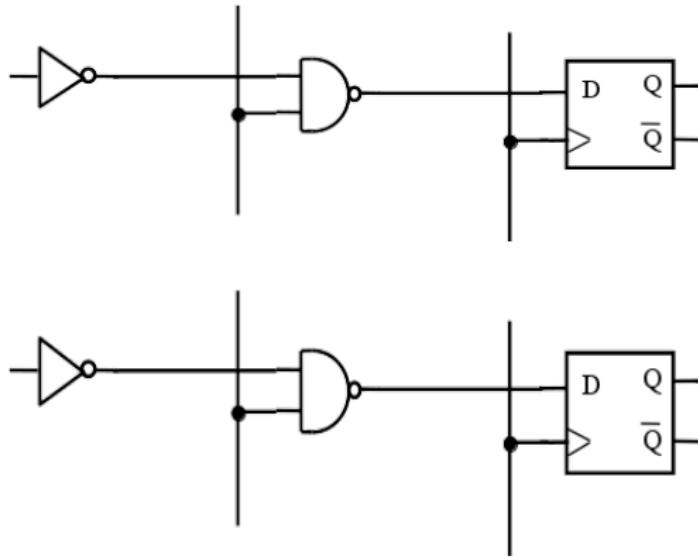


- All cells have same height
- Power supply and Ground connected by abutment.
- Cell design should be free of DRC error.
- Any abutment of any couple of cells should be free of DRC error.
- Wiring inside cell limited to Metal1 level.

Standard cell principles

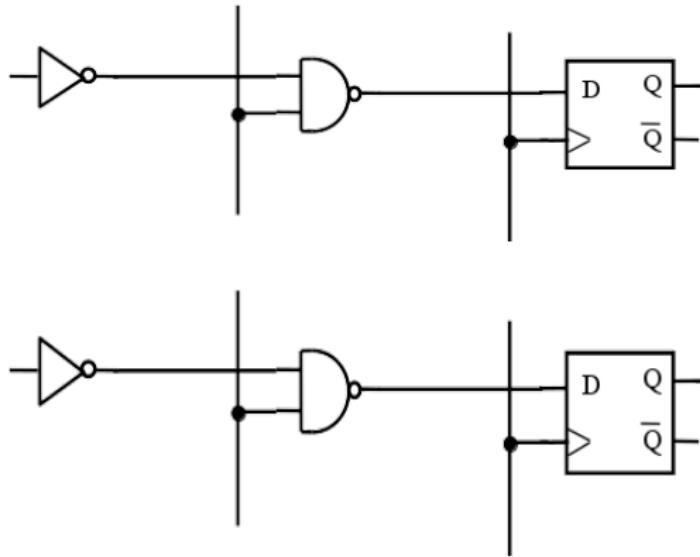

- All cells have same height
- Power supply and Ground connected by abutment.
- Cell design should be free of DRC error.
- Any abutment of any couple of cells should be free of DRC error.
- Wiring inside cell limited to Metal1 level.


Standard cell principles

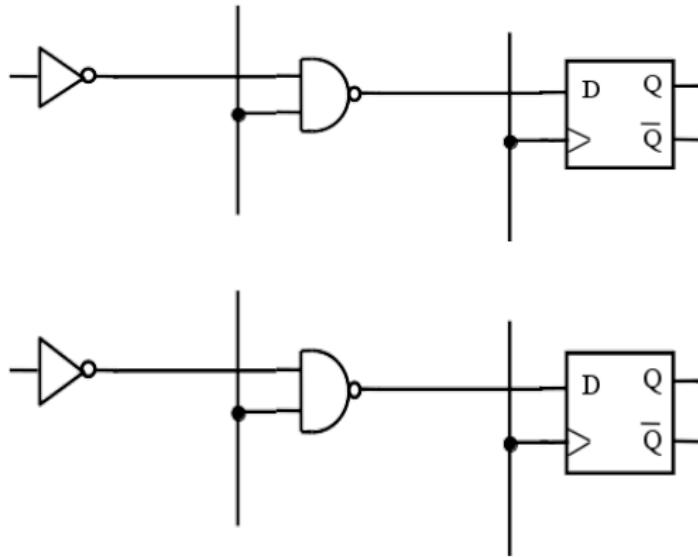

- All cells have same height
- Power supply and Ground connected by abutment.
- Cell design should be free of DRC error.
- Any abutment of any couple of cells should be free of DRC error.
- Wiring inside cell limited to Metal1 level.



Reference technology profile

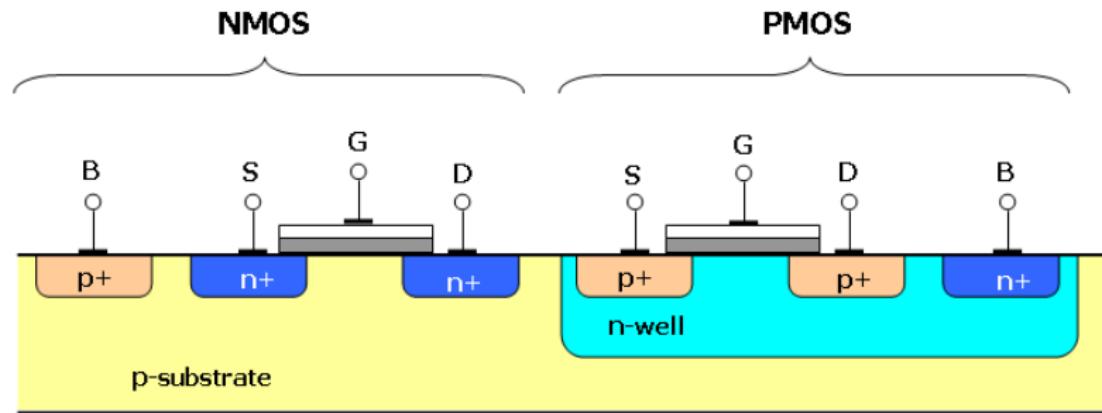




gpdk045 standard cell template

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nlmp
	Phvt
	Plvt
	Nzvt
	SiProt
	Cont
	Metal1

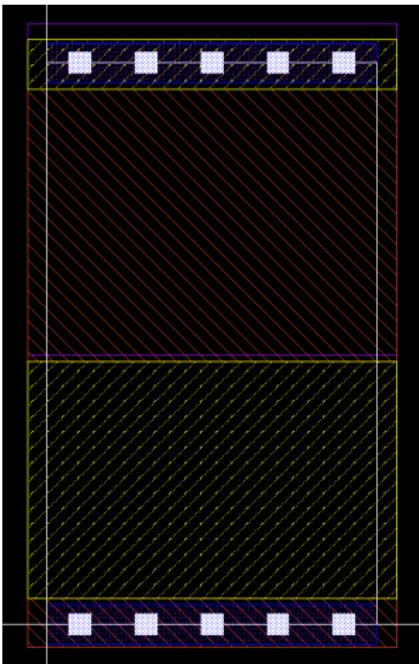


- NMOS areas and PMOS areas already filled.
- Body-ties areas for NMOS and PMOS already filled
- Body-ties already connected to V_{dd} (for PMOS) or V_{ss} (for NMOS)
- Simple abutment of cells fill an raw of cells with NMOS and PMOS areas.



gpdk045 standard cell template

practical design

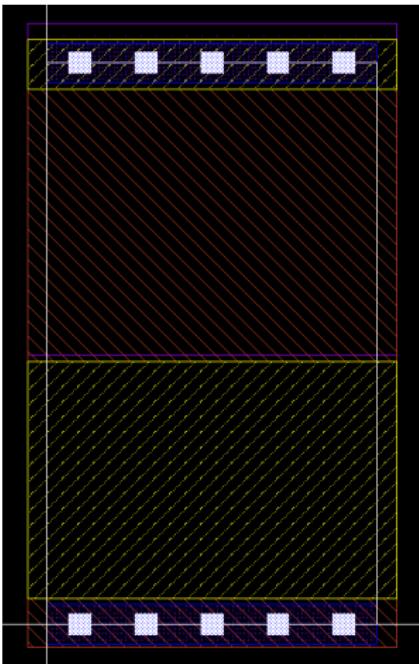Nwell
Oxide
Oxide_thk
Poly
Pimp
Nhvt
Nlvt
Nlmp
Phvt
Plvt
Nzvt
SiProt
Cont
Metal1




- NMOS areas and PMOS areas already filled.
- Body-ties areas for NMOS and PMOS already filled
- Body-ties already connected to V_{dd} (for PMOS) or V_{ss} (for NMOS)
- Simple abutment of cells fill an raw of cells with NMOS and PMOS areas.



gpdk045 standard cell template

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nlmp
	Phvt
	Plvt
	Nzvt
	SiProt
	Cont
	Metal1

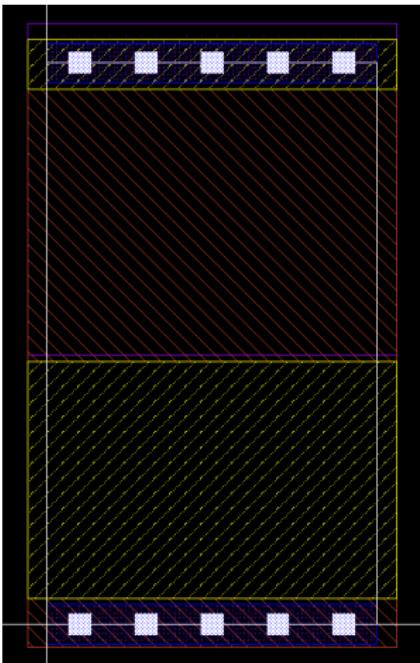


- NMOS areas and PMOS areas already filled.
- Body-ties areas for NMOS and PMOS already filled
- Body-ties already connected to V_{dd} (for PMOS) or V_{ss} (for NMOS)
- Simple abutment of cells fill an raw of cells with NMOS and PMOS areas.



gpdk045 standard cell template

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nlmp
	Phvt
	Plvt
	Nzvt
	SiProt
	Cont
	Metal1

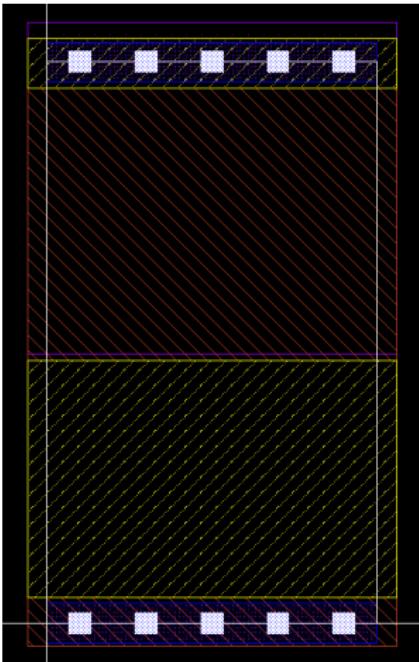


- NMOS areas and PMOS areas already filled.
- Body-ties areas for NMOS and PMOS already filled
- Body-ties already connected to V_{dd} (for PMOS) or V_{ss} (for NMOS)
- Simple abutment of cells fill an raw of cells with NMOS and PMOS areas.



gpdk045 adder

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Pvt
	Nzvt
	SiProt
	Cont
	Metal1

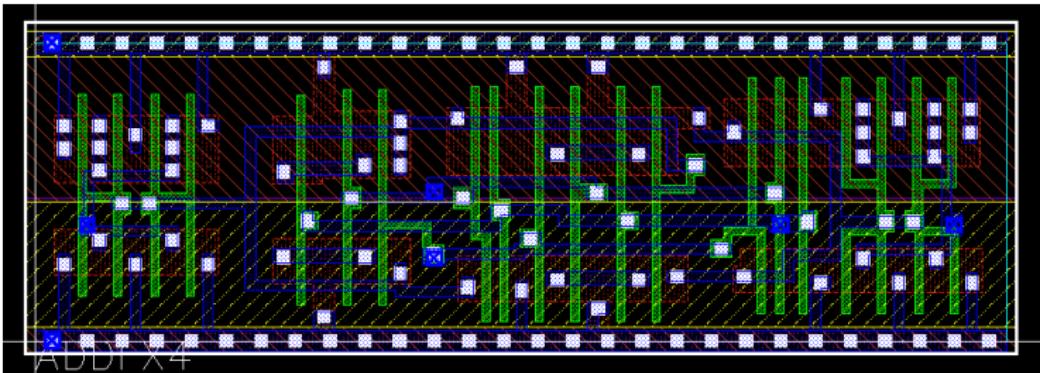


- All transistors have horizontal orientation.
- Maximal width defined by NMOS and PMOS areas height.
- Use parallel transistors for larger widths.
- Drain/Source implants may be used for local short wires (beware the resistivity).
- Global optimisation of Eulerian Paths (N(P)MOS subcircuits are graphs which visits every edge exactly once)

gdk045 adder

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Plvt
	Nzvt
	SiProt
	Cont
	Metal1

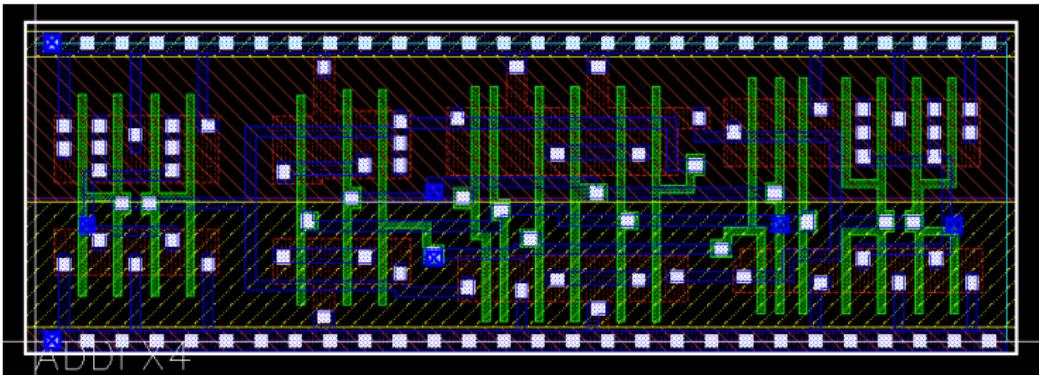


- All transistors have horizontal orientation.
- Maximal width defined by NMOS and PMOS areas height.
- Use parallel transistors for larger widths.
- Drain/Source implants may be used for local short wires (beware the resistivity).
- Global optimisation of Eulerian Paths (N(P)MOS subcircuits are graphs which visits every edge exactly once)

gdk045 adder

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Plvt
	Nzvt
	SiProt
	Cont
	Metal1

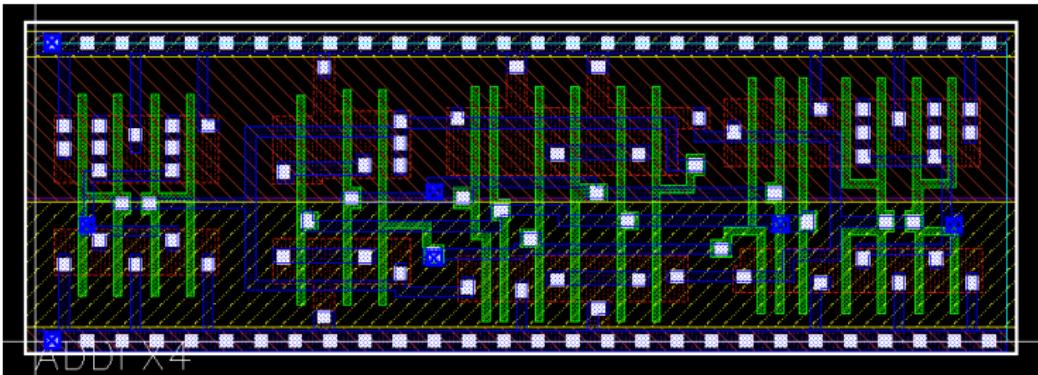


- All transistors have horizontal orientation.
- Maximal width defined by NMOS and PMOS areas height.
- Use parallel transistors for larger widths.
- Drain/Source implants may be used for local short wires (beware the resistivity).
- Global optimisation of Eulerian Paths (N(P)MOS subcircuits are graphs which visits every edge exactly once)

gdk045 adder

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Plvt
	Nzvt
	SiProt
	Cont
	Metal1

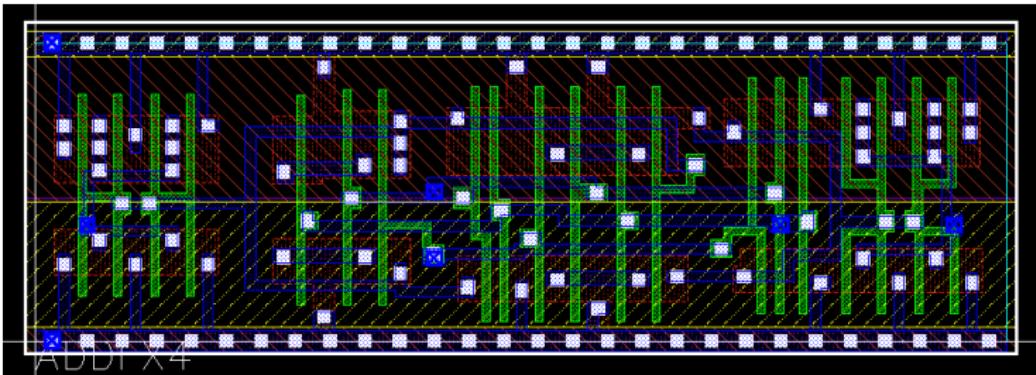


- All transistors have horizontal orientation.
- Maximal width defined by NMOS and PMOS areas height.
- Use parallel transistors for larger widths.
- Drain/Source implants may be used for local short wires (beware the resistivity).
- Global optimisation of Eulerian Paths (N(P)MOS subcircuits are graphs which visits every edge exactly once)

gdk045 adder

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Pvt
	Nzvt
	SiProt
	Cont
	Metal1

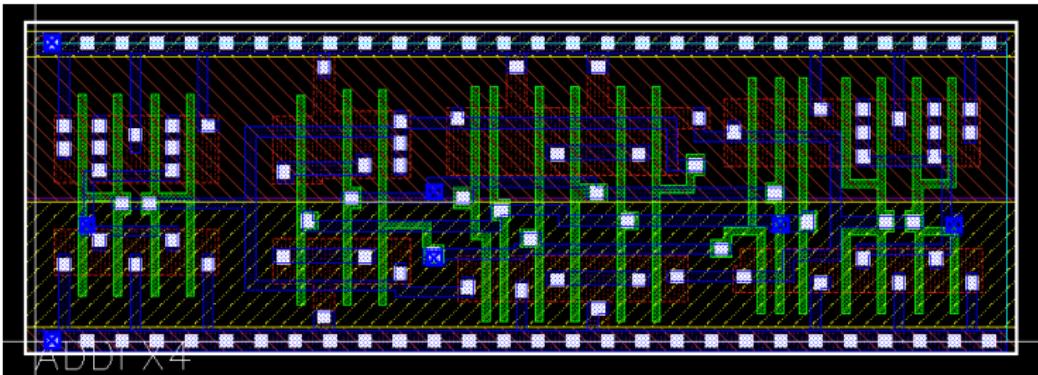


- All transistors have horizontal orientation.
- Maximal width defined by NMOS and PMOS areas height.
- Use parallel transistors for larger widths.
- Drain/Source implants may be used for local short wires (beware the resistivity).
- Global optimisation of Eulerian Paths (N(P)MOS subcircuits are graphs which visits every edge exactly once)



gpdk045 adder abstract

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Pvt
	Nzvt
	SiProt
	Cont
	Metal1

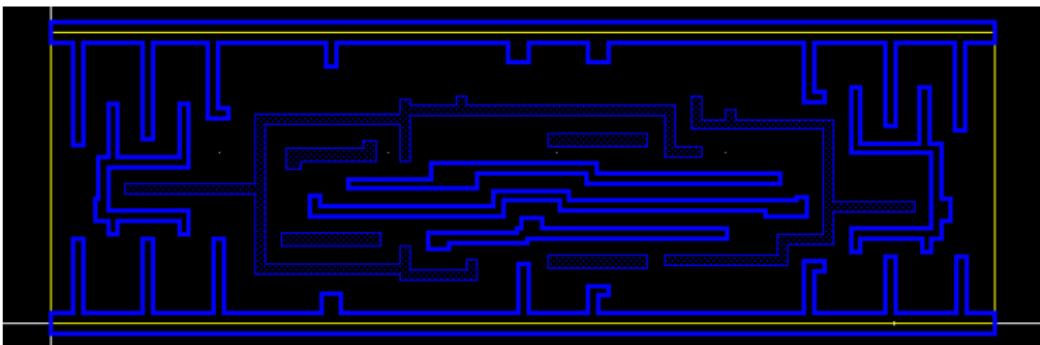


- Only needed informations for Place and Route.
- Wires connected to Input/Output pins of the cell
- Wires that are obstacles for wiring
- The router may use Metal1 has a wiring layer if enough room inside the cell



gpdk045 adder abstract

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Pvt
	Nzvt
	SiProt
	Cont
	Metal1

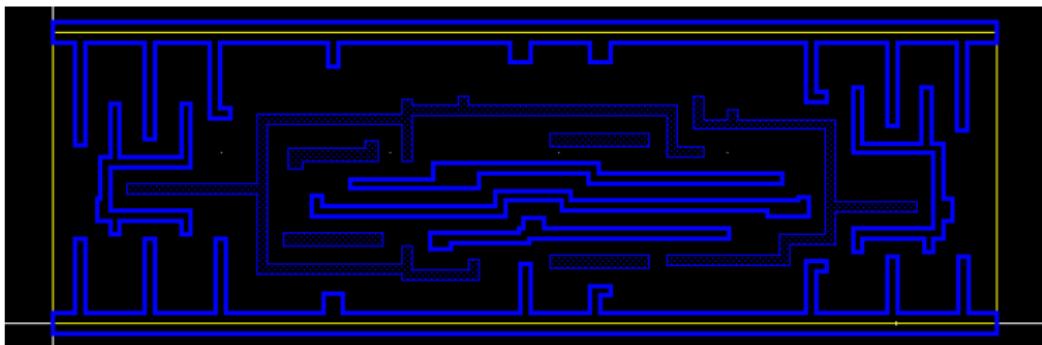


- Only needed informations for Place and Route.
- Wires connected to Input/Output pins of the cell
- Wires that are obstacles for wiring
- The router may use Metal1 has a wiring layer if enough room inside the cell



gpdk045 adder abstract

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Pvt
	Nzvt
	SiProt
	Cont
	Metal1

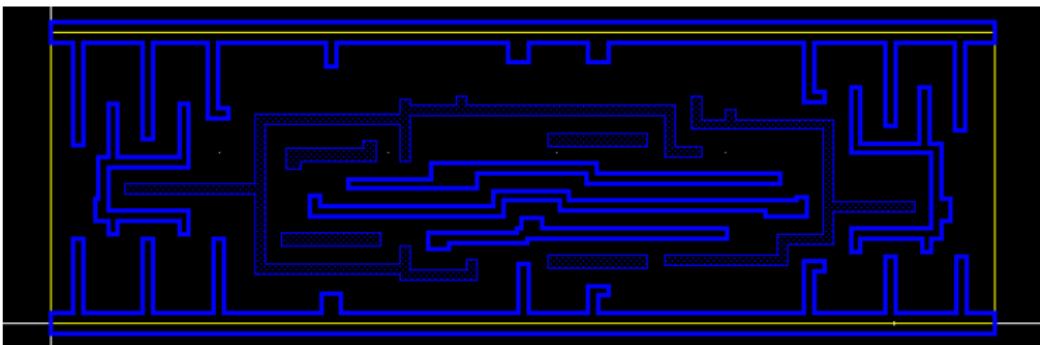


- Only needed informations for Place and Route.
- Wires connected to Input/Output pins of the cell
- Wires that are obstacles for wiring
- The router may use Metal1 has a wiring layer if enough room inside the cell



gpdk045 adder abstract

practical design

	Nwell
	Oxide
	Oxide_thk
	Poly
	Pimp
	Nhvt
	Nlvt
	Nimp
	Phvt
	Pvt
	Nzvt
	SiProt
	Cont
	Metal1

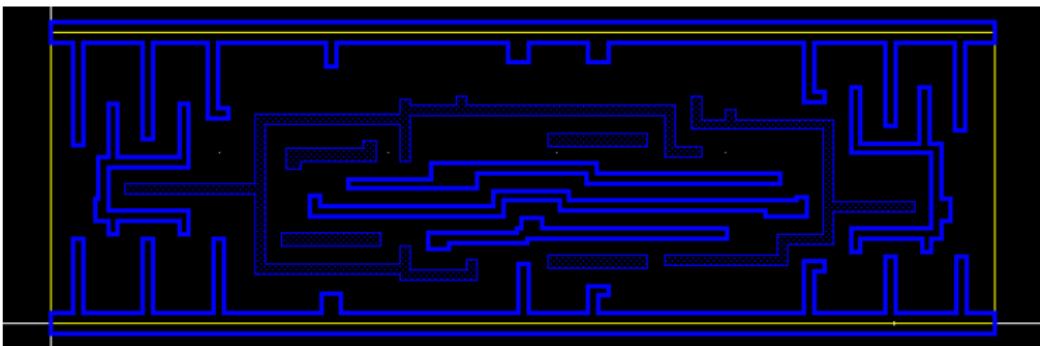

- Only needed informations for Place and Route.
- Wires connected to Input/Output pins of the cell
- Wires that are obstacles for wiring
- The router may use Metal1 has a wiring layer if enough room inside the cell



Outline

Dynamic logic

Differential logic

Application specific logic

Performance optimization


Sequential cells

Standard cell design

Practical work

Dynamic positive edge-triggered D flip-flop


TSPC : True Single Phase Clock logic

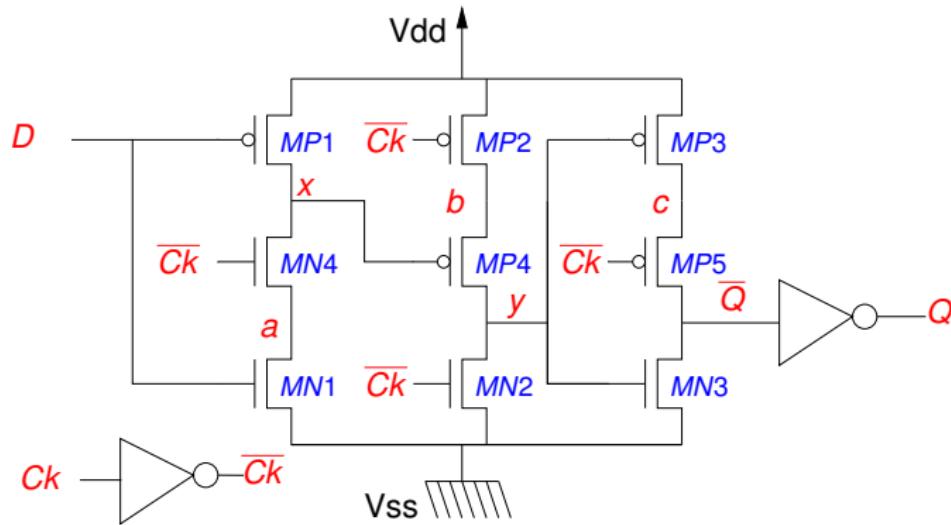

- Very compact structure.
- Supposed to be faster than standard CMOS cell.

Dynamic positive edge-triggered D flip-flop

TSPC : True Single Phase Clock logic

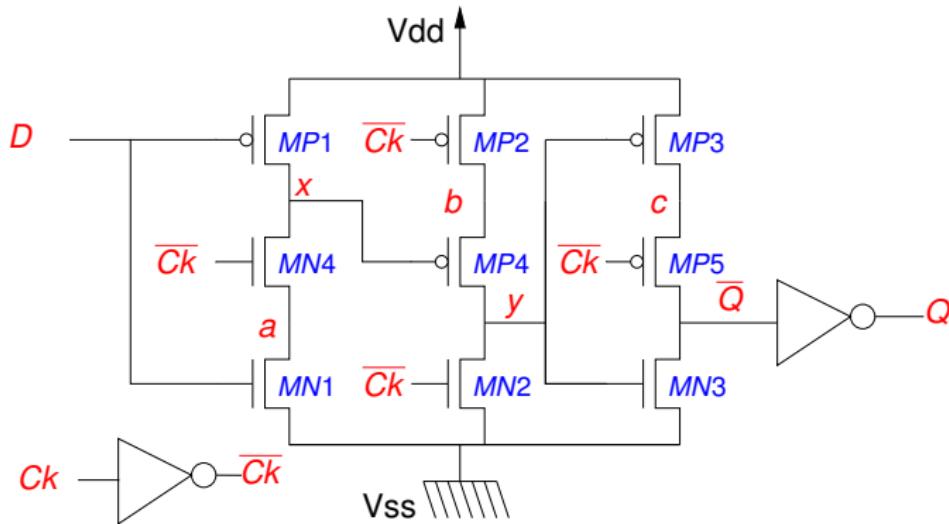


- Very compact structure.
- Supposed to be faster than standard CMOS cell.

Dynamic positive edge-triggered D flip-flop

Homework

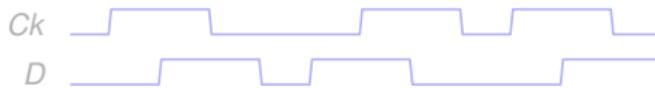- Question : How does this cell works ?
- Setup a table D, Q, Ck and all internal nodes of the cell.
- Add also the states of the MOS transistors (ON or OFF).
- Each internal node may have the states 0, 1, U(Unknown), Z0 (high-impedance 0), Z1 (high-impedance 1), or ZU (high-impedance Unknown).
- Imagine the following input sequence.




- Fill the table with the successive values of the signals
- Check if the cell is a D flip-flop.

Dynamic positive edge-triggered D flip-flop

Homework

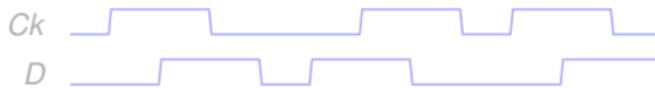- Question : How does this cell works ?
- Setup a table D, Q, Ck and all internal nodes of the cell.
- Add also the states of the MOS transistors (ON or OFF).
- Each internal node may have the states 0, 1, U(Unknown), Z0 (high-impedance 0), Z1 (high-impedance 1), or ZU (high-impedance Unknown).
- Imagine the following input sequence.




- Fill the table with the successive values of the signals
- Check if the cell is a D flip-flop.

Dynamic positive edge-triggered D flip-flop

Homework

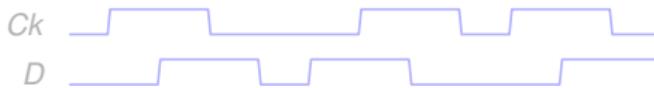- Question : How does this cell works ?
- Setup a table D, Q, Ck and all internal nodes of the cell.
- Add also the states of the MOS transistors (ON or OFF).
- Each internal node may have the states 0, 1, U(Unknown), Z0 (high-impedance 0), Z1 (high-impedance 1), or ZU (high-impedance Unknown).
- Imagine the following input sequence.




- Fill the table with the successive values of the signals
- Check if the cell is a D flip-flop.

Dynamic positive edge-triggered D flip-flop

Homework

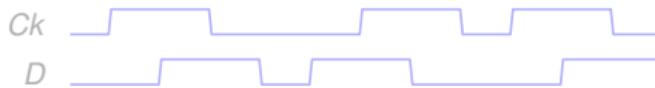- Question : How does this cell works ?
- Setup a table D, Q, Ck and all internal nodes of the cell.
- Add also the states of the MOS transistors (ON or OFF).
- Each internal node may have the states 0, 1, U(Unknown), Z0 (high-impedance 0), Z1 (high-impedance 1), or ZU (high-impedance Unknown).
- Imagine the following input sequence.




- Fill the table with the successive values of the signals
- Check if the cell is a D flip-flop.

Dynamic positive edge-triggered D flip-flop

Homework

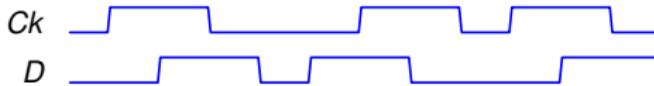- Question : How does this cell works ?
- Setup a table D, Q, Ck and all internal nodes of the cell.
- Add also the states of the MOS transistors (ON or OFF).
- Each internal node may have the states 0, 1, U(Unknown), Z0 (high-impedance 0), Z1 (high-impedance 1), or ZU (high-impedance Unknown).
- Imagine the following input sequence.




- Fill the table with the successive values of the signals
- Check if the cell is a D flip-flop.

Dynamic positive edge-triggered D flip-flop

Homework

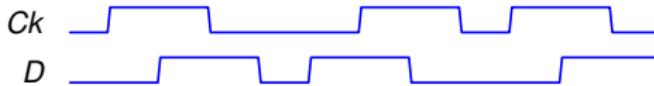- Question : How does this cell works ?
- Setup a table D, Q, Ck and all internal nodes of the cell.
- Add also the states of the MOS transistors (ON or OFF).
- Each internal node may have the states 0, 1, U(Unknown), Z0 (high-impedance 0), Z1 (high-impedance 1), or ZU (high-impedance Unknown).
- Imagine the following input sequence.




- Fill the table with the successive values of the signals
- Check if the cell is a D flip-flop.

Dynamic positive edge-triggered D flip-flop

Homework

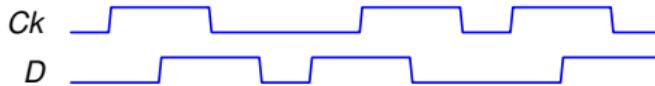- Question : How does this cell works ?
- Setup a table D, Q, Ck and all internal nodes of the cell.
- Add also the states of the MOS transistors (ON or OFF).
- Each internal node may have the states 0, 1, U(Unknown), Z0 (high-impedance 0), Z1 (high-impedance 1), or ZU (high-impedance Unknown).
- Imagine the following input sequence.



- Fill the table with the successive values of the signals
- Check if the cell is a D flip-flop.